

# Memory Subsystem

Ashish Kuvelkar  
Hardware Technology Development Group  
C-DAC, Pune

# Memory

Why is the memory required?

- Temporary storage
- Break the problem in time domain

How the data can be stored ?

- Charge
- Voltage
- Mechanical action
- Light
- Magnetisation

# Memory

What is the choice criteria ?


- Basic
  - Reliability
  - Size
  - Speed
  - Power
  - Type of use
- Secondary
  - Package type,
  - cost, availability,
  - Scalability
  - voltage compatibility(3.3/5V)

# Memory

What are the components ?


- Basic
  - Storage element
  - Address decoder
  - Data line driver
- Optional
  - Data multiplexers
  - Sense amplifiers
  - Voltage equalizers
  - Refresh circuits

# Memory Types

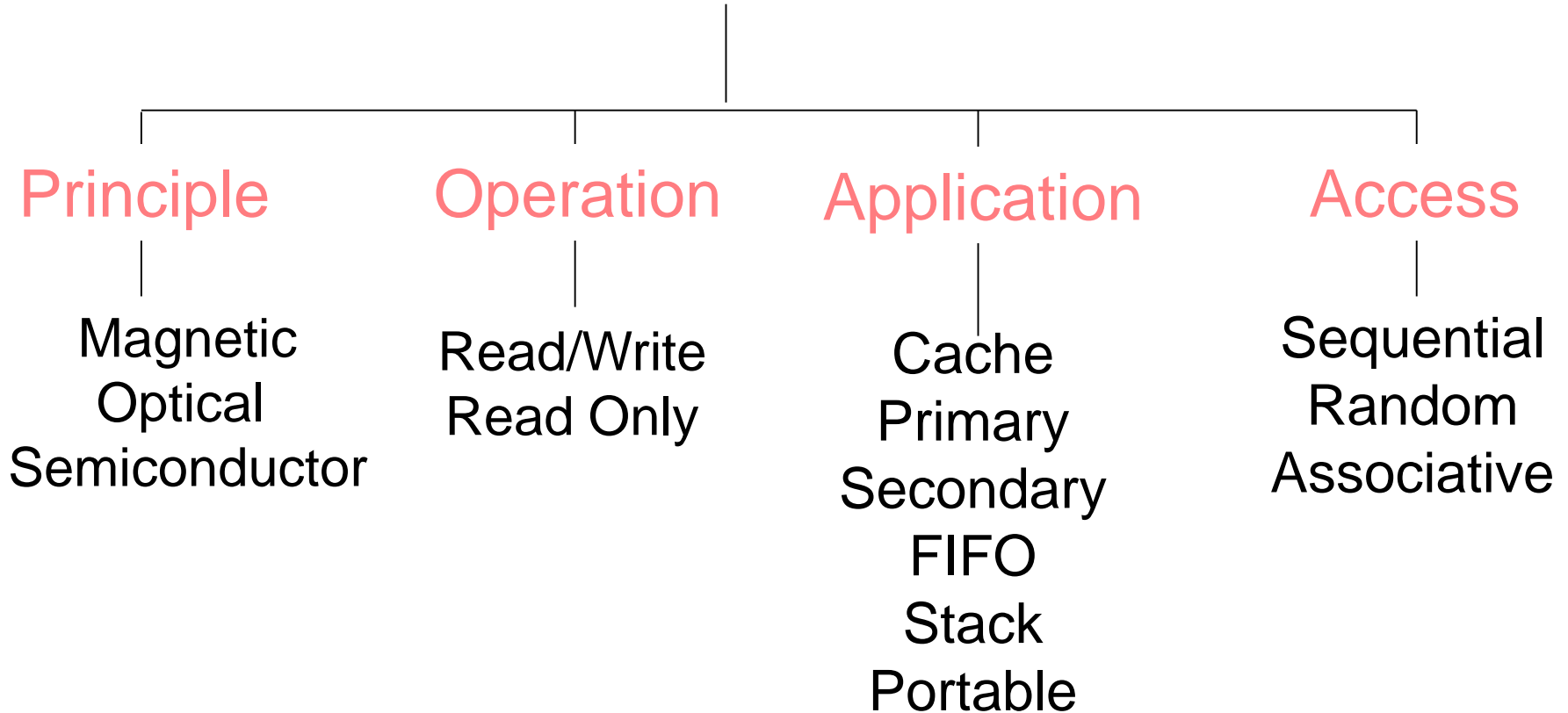
 
# Read-Only Memory (ROM)

- A combinational circuit with  $n$  inputs and  $b$  outputs:



- Programmable - values determined by user
- Nonvolatile - contents retained without power

# Read-Only Memory (ROM)

- Two views:
  - ROM stores  $2^n$  words of  $b$  bits each, or
  - ROM stores an  $n$ -input,  $b$ -output truth table

Example:


$n = 2$		$b = 4$			
A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	1	1	1
1	0	0	1	1	1
1	1	1	0	1	0

← Stores 4 4-bit words, or  
stores 4 functions of 2  
input variables

# Using ROMs for Combinational Logic

A 3-input, 4-output combinational logic function:

Inputs			Outputs			
A2	A1	A0	D3	D2	D1	D0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

Function: 2-to-4 Decoder with Polarity Control


A2 = Polarity (0 = active Low, 1= active High)

A1, A0 = I1, I0 (2-bit input )


D3...D0 = Y3...Y0 (4-bit decoded output)



# Equivalent Decoder in Discrete Logic

 


# Internal Structure of 4×4 Diode ROM


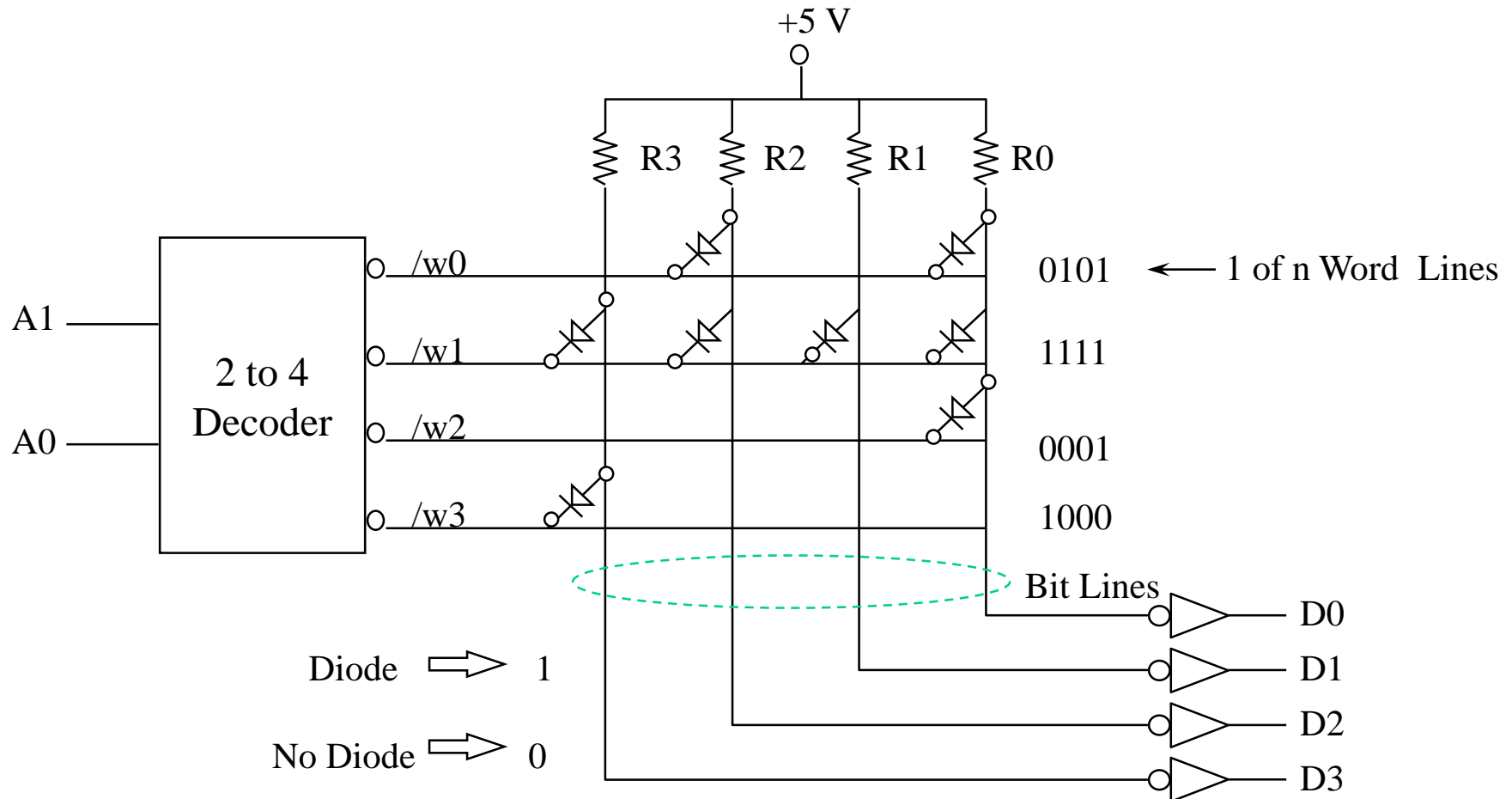

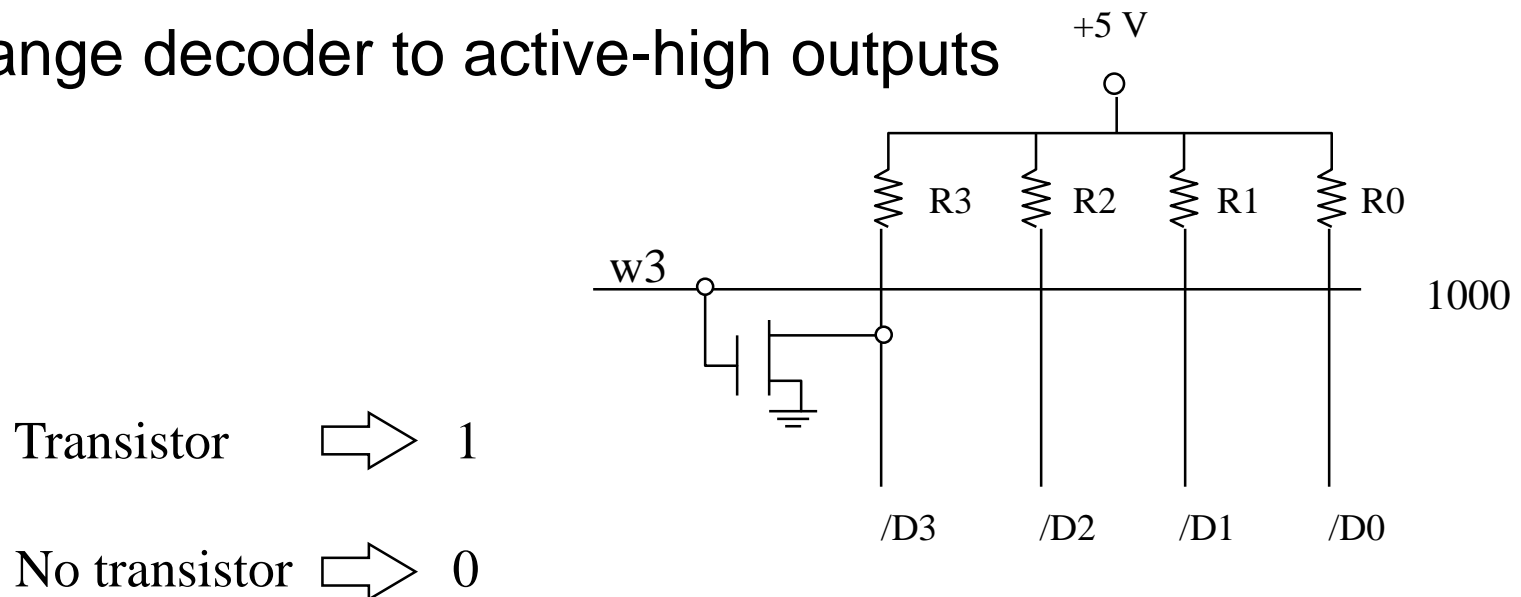
# Internal Structure of MOS Transistor ROM

- Replace diodes with MOS transistors
- Change decoder to active-high outputs




# Consider a 64 x 1 ROM

 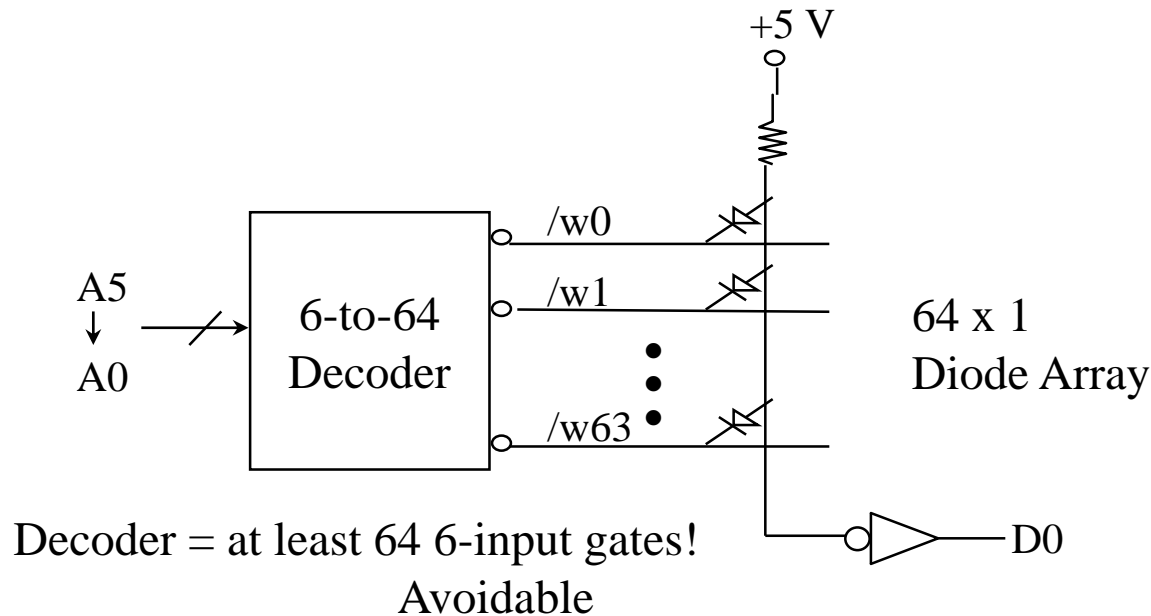


→ Very tall, narrow chip (BAD)  
Even worse for larger chips!  
How to make it more square?


# 2-Dimensional Decoding

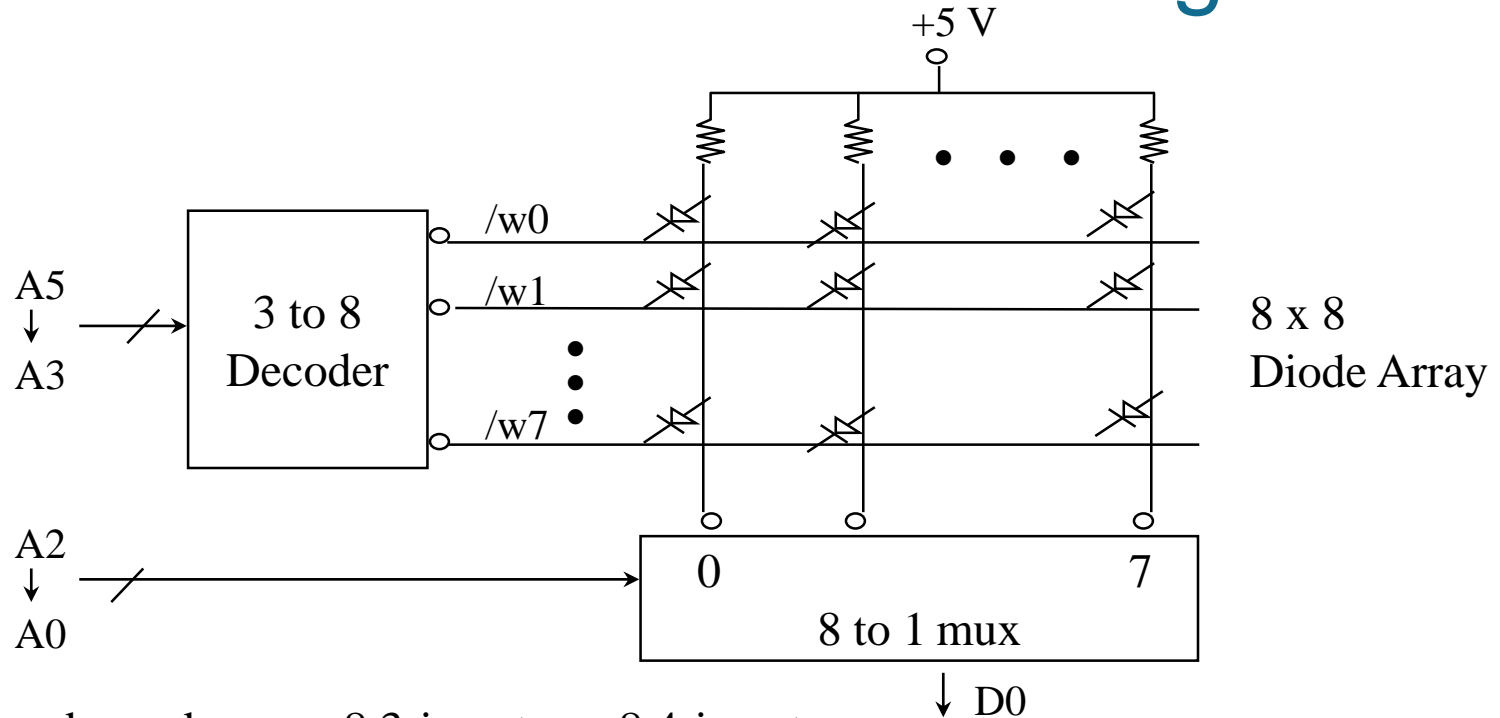

 Decoder and mux = 8 3-in gates + 8 4-in gates




# 64K x 8 ROM with 2-D Decoding

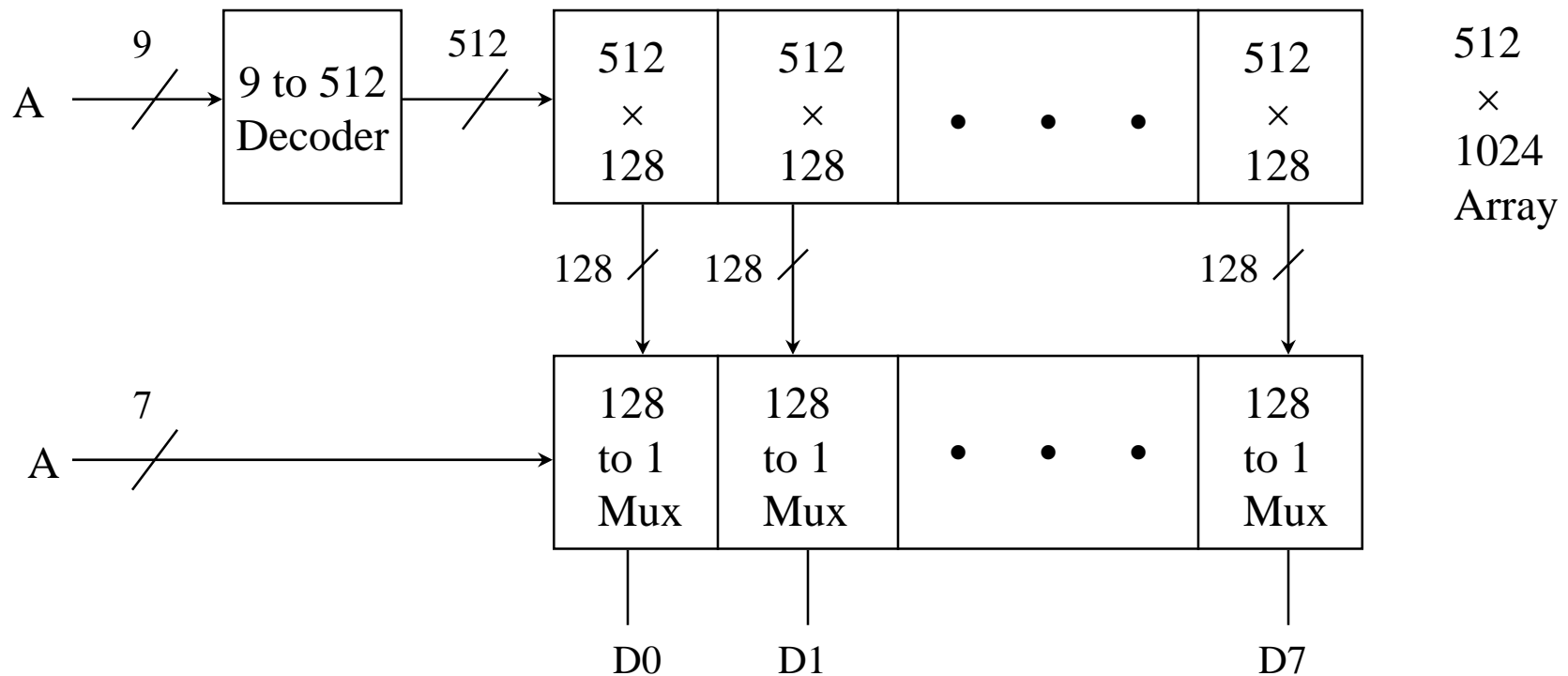

 
# Types Of ROMs (1)

- Mask ROM
  - Connections made by the semiconductor vendor
  - Expensive setup cost
  - Several weeks for delivery
  - High volume only
  - Bipolar or MOS technology





 - PROM
  - Programmable ROM
  - Connections made by equipment manufacturer
  - Vaporize (blow) fusible links with PROM programmer using high voltage/current pulses
  - Bipolar technology
  - One-time programmable


  
## Types of ROMs (2)

- EPROM
  - Erasable Programmable ROM
  - Charge trapped on extra “floating gate” of MOS transistors
  - Exposure to UV light removes charge
    - 10-20 minutes
    - Quartz Lid = expensive package
  - Limited number of erasures (10-100)
- EEPROM (E<sup>2</sup>ROM)
  - Electrically Erasable ROM
  - Floating gates charged/discharged electrically
  - Not RAM! (relatively slow charge/discharge)
  - limited number of charge/discharge cycles (10,000)






## Types of ROMs (3)

- Flash Memory
  - Electronically erasable in blocks
  - 100,000 erase cycles
  - Simpler and denser than EEPROM

# EPROM and EEPROM Structure

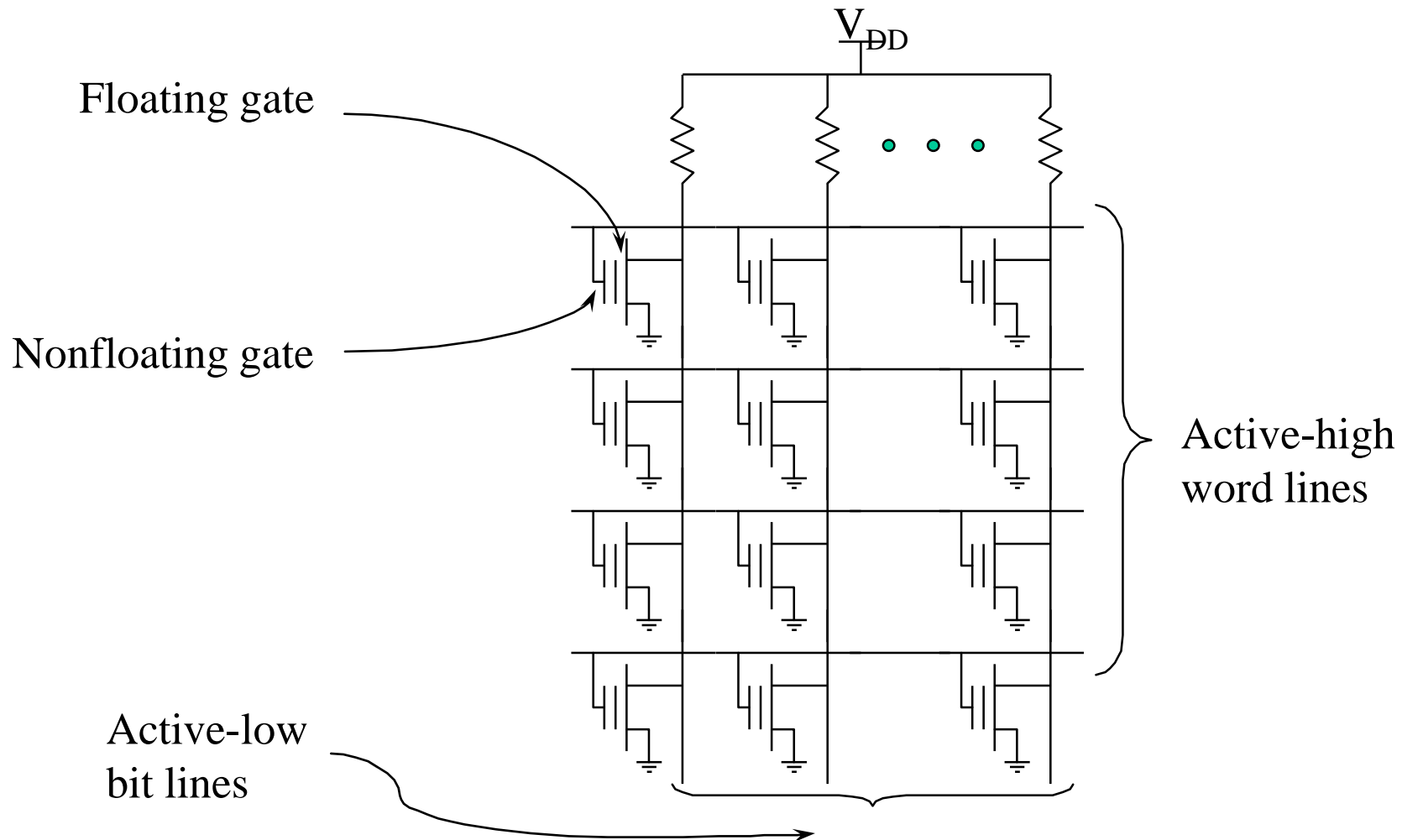

# NOR Vs. NAND Flash

Introduced by	Intel in 1988	Toshiba in 1989
Capacity	1 to 16MB	8 to 128MB
Code Execution	Yes	No
Erase	Very Slow(5 Sec)	Fast (3 msec)
Write	Slow	Fast
Read	Fast	Fast
Erase cycle	10k – 100k	100K to 1M
Interface	Memory like	I/O only
Access	Random	Sequential
Ideal usage	Code Storage	Basic data storage

# ROM Type Summary

Type	Technology	Read Cycle	Write Cycle	Comments
Mask ROM	NMOS, CMOS	20-200 ns	4 weeks	Write once; low power
Mask ROM	Bipolar	<100 ns	4 weeks	Write once; high power; low density
PROM	Bipolar	<100 ns	5 minutes	Write once; high power; no mask charge
EPROM	NMOS, CMOS	25-200 ns	5 minutes	Reusable; low power; no mask charge
EEPROM	NMOS	50-200 ns	10 $\mu$ s/byte	10,000 writes/location limit
FLASH	CMOS	25-200 ns	10 $\mu$ s/block	100,000 erase cycles

# Read/Write Memory (RWM / RAM)

- RWM = RAM (Random Access Memory)
- Highly structured like ROM's and PLD's
- Can store and retrieve data at the same speed
- Static RAM (SRAM) retains data in latches (while powered)
- Dynamic RAM (DRAM) stores data as capacitor charge; all capacitors must be recharged periodically.
- Volatile Memory: Both Static and Dynamic RAM
- Nonvolatile Memory: Data retained when power lost  
ROM's, NVRAM (w/battery), FlashMemory

# Random Access Memory

Types

SRAM , DRAM

Application

Primary memory, Cache , FIFO , STACK


Speed

Access Typical – 10 – 100 ns

Size


100's of KBs to 10's of MBs

# Basic Structure of SRAM

 

- Address/Control/Data Out lines like a ROM (Reading)  
+ Write Enable (WE) and Data In (DIN) (Writing)

# One Bit of SRAM

 


- SEL and WR asserted → IN data stored in D-latch (Write)
- SEL only asserted → D-latch output enabled (Read)
- SEL not asserted → No operation



# Structure of 8x4 SRAM

- 3-to-8 Decoder selects one row of cells for Read or Write
- If ADDR + CS + OE are asserted, DOUT (3-0) is enabled. (Read)
- If ADDR + DIN + CS + WE are asserted, DIN → latches (Write)


# 8 x 4 SRAM

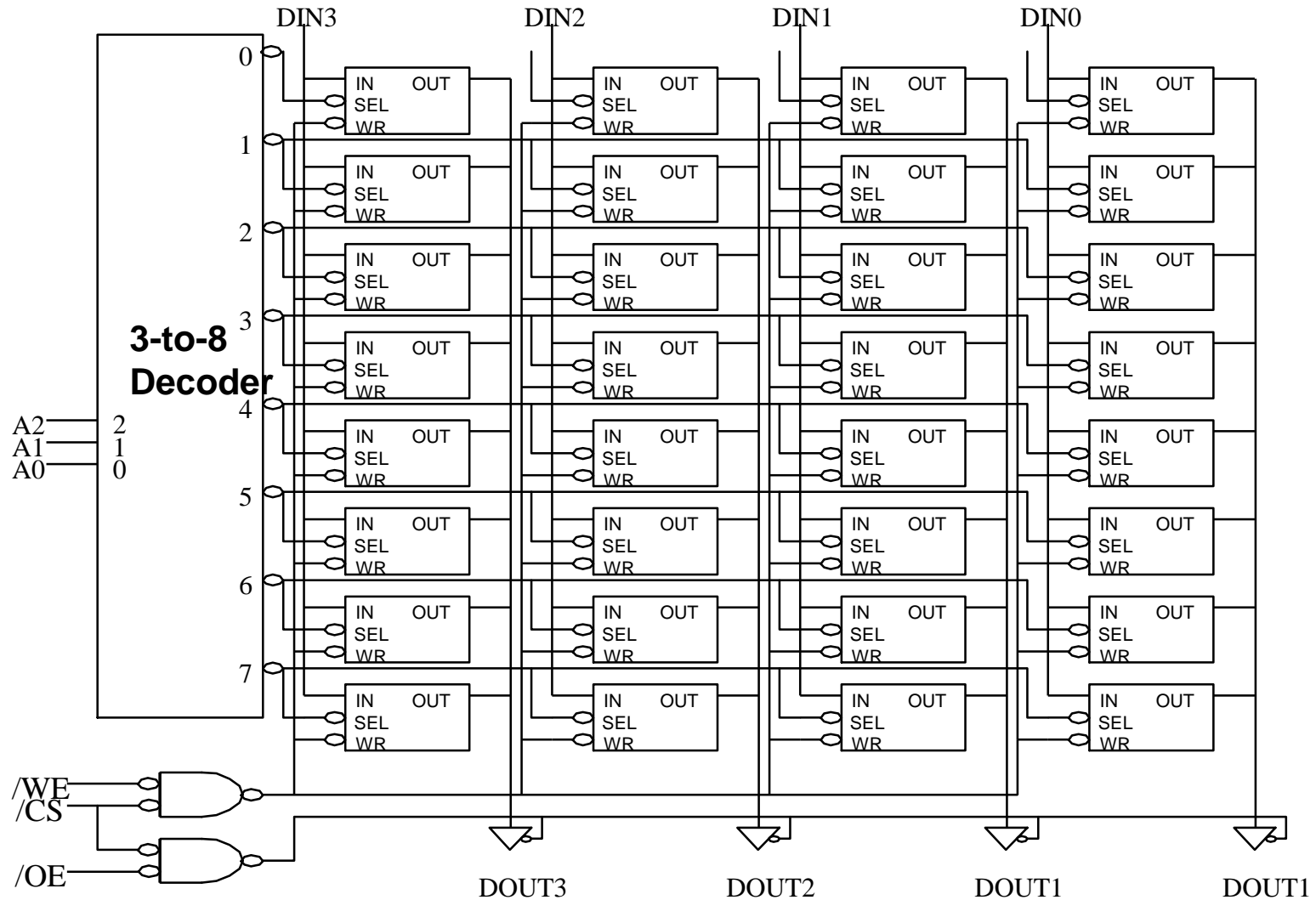

# SRAM Timing

- During READ, outputs are combinational functions of ADDR, CS, OE (like ROM)
  - Inputs can freely change without problems (except for propagation delay from last input change to output)
- During WRITE, data stored in latches
  - Thus, Setup & Hold on Data IN relative to trailing edge of /WR
- ADDR must be stable
  - for setup time before /WR asserted, and
  - for hold time after /WR deasserted
    - to prevent “spraying” data to multiple rows
- /WR asserted when BOTH /CS and /WE asserted
- /WR deasserted when EITHER /CS or /WE deasserted

# READ Timing (SRAM)

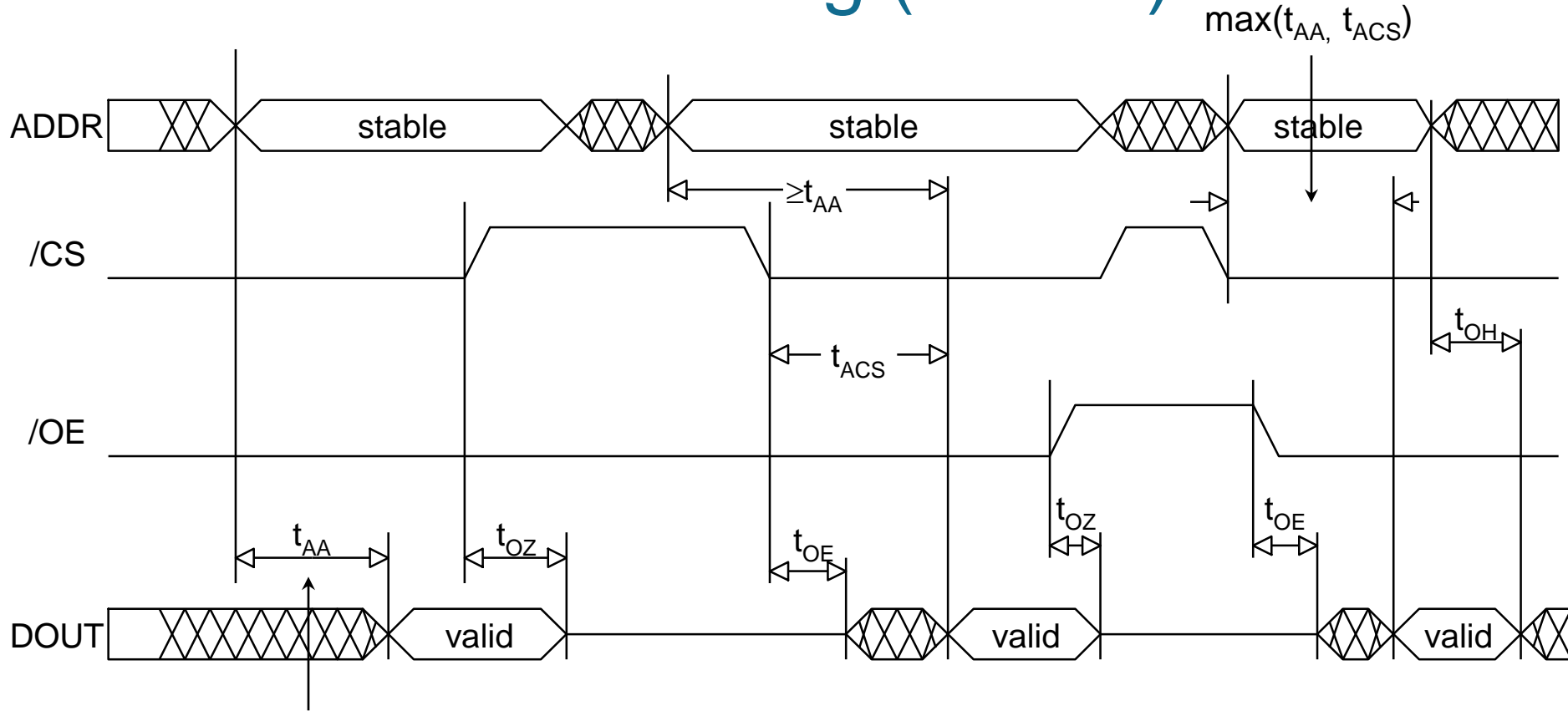


Primary Spec  
for SRAMs

# WRITE Timing (SRAM)

(WE-controlled write)

(CS-controlled write)

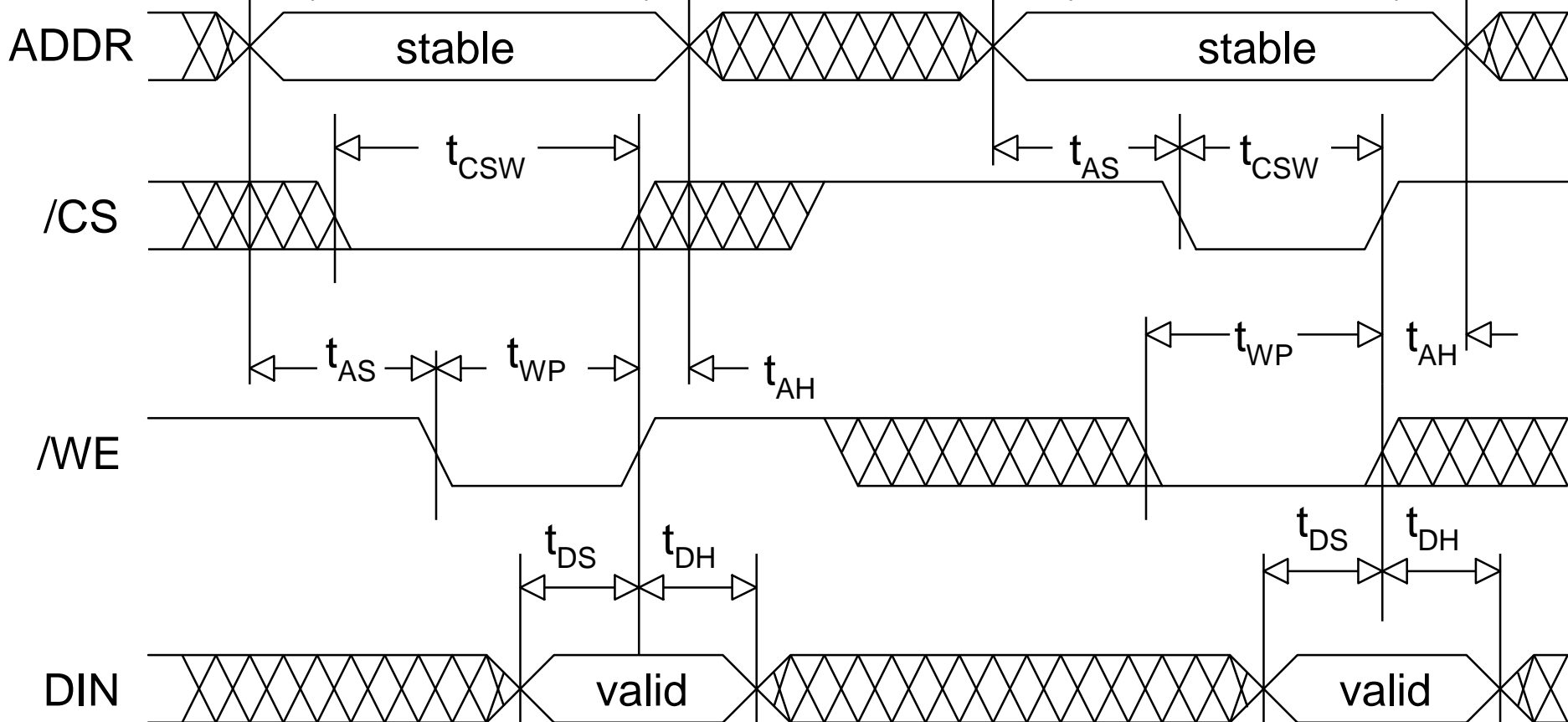



# SRAM-Read/Write

Asynchronous SRAM

Address Before Cycle Start

Read data valid only after  
/OE Asserted

Write Initiated by either  
/CE or /WE

Write Terminated by either  
/CE or /WE

# SRAM Types

## Asynchronous

Read , Write Cycles controlled by /CE,/WE,/OE.

## Synchronous and Sync-Burst

Clock with /WE , /OE controls data cycles.

## Double-Data SRAM

Data read and written on both edges of clock.

## Quad-Data SRAM

Dual-Unidirectional Ports with both edges to read/write.


## Zero Bus Turn-around RAM

No Additional wait required between read and write.



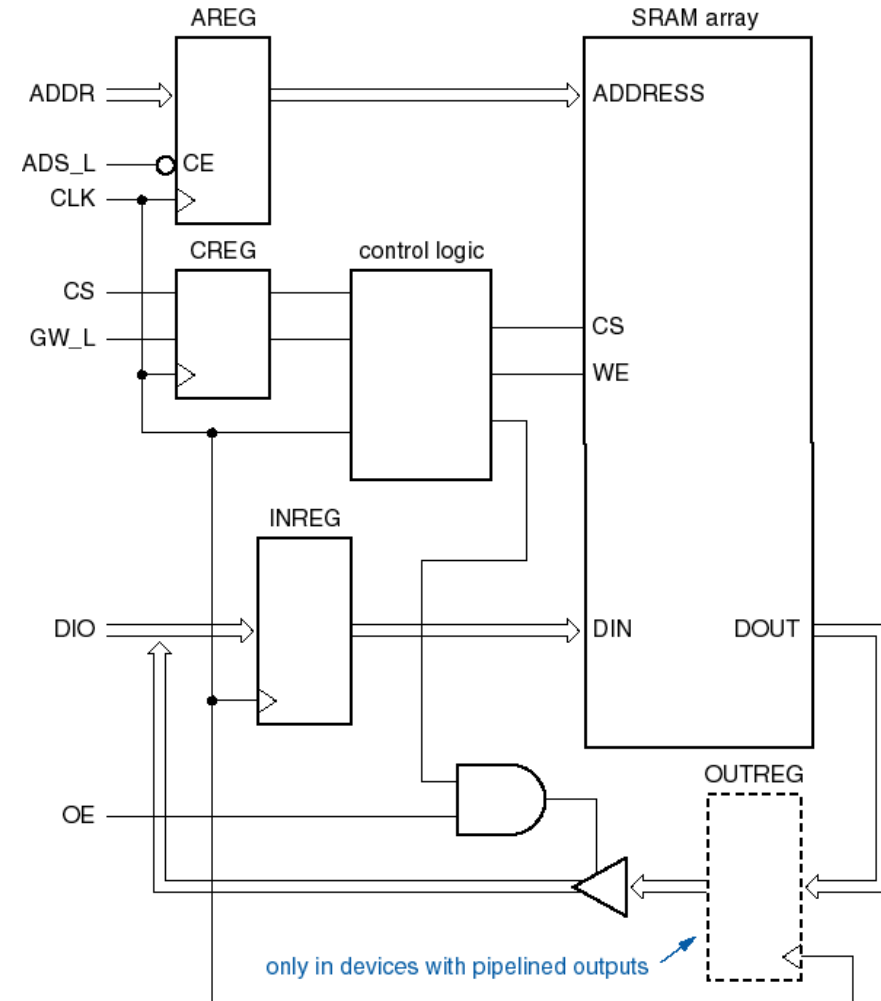
# Synchronous SRAMs

- Use latch-type SRAM cells internally
- Put registers in front of address control and data for easier interfacing with synchronous systems at high speeds
- OUTREG is present for pipelined output
  - Absent for flow through outputs



# SSRAM Read –Flow through

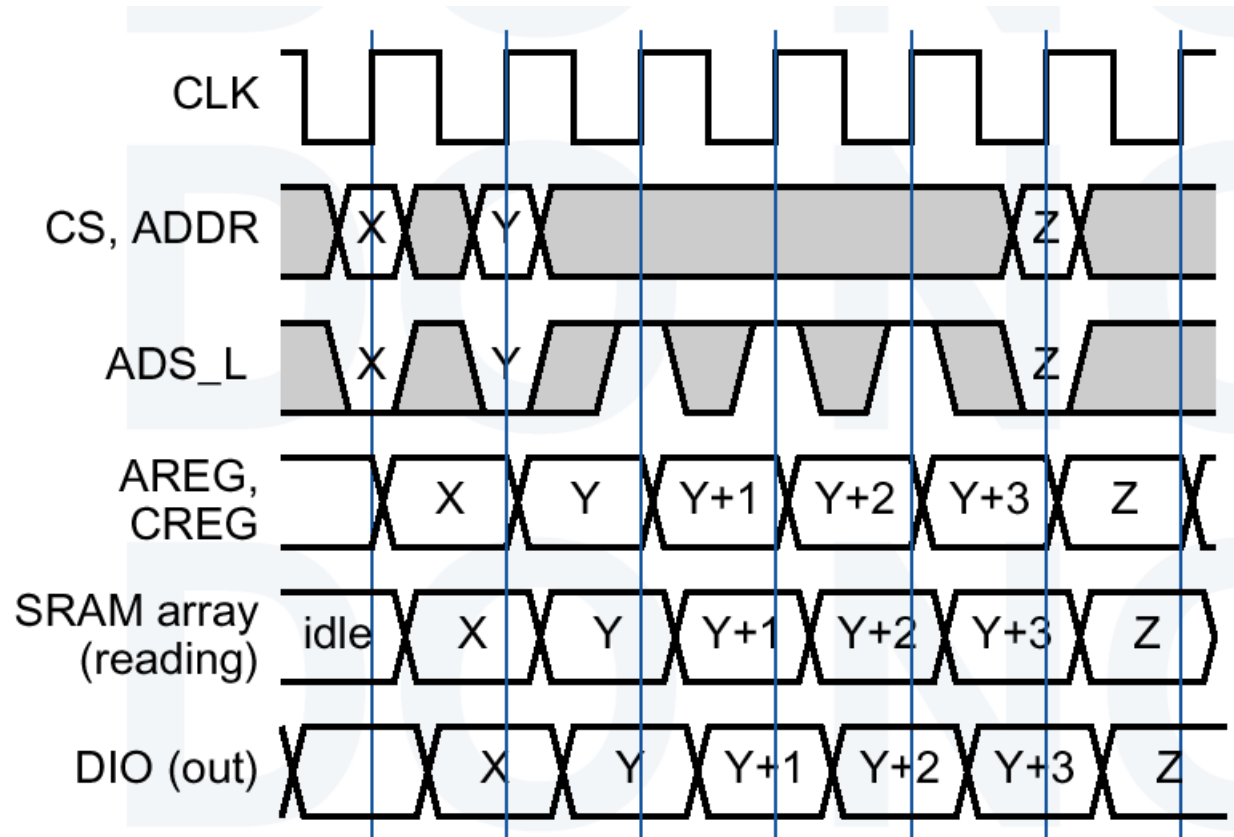

Note: GW\_L is HIGH throughout


# Read Operation

- Control and address inputs sampled at rising edge
- AREG loaded only if ADS\_L is asserted
- During the next clock the internal SRAM is accessed and data is delivered to DIO pins
- Burst mode is supported
  - AREG behaves like a counter


# Write Operation

- Control and address inputs sampled at rising edge
- Data is stored temporarily in INREG
- During the next clock the internal SRAM is written when the control signal GW\_L is asserted
  - ADS\_L should be inhibited for one clock after loading the address
- Burst mode is supported
  - AREG behaves like a counter
- It is not possible to write at two non-sequential addresses in successive clocks.

# SSRAM Write – Flow Through

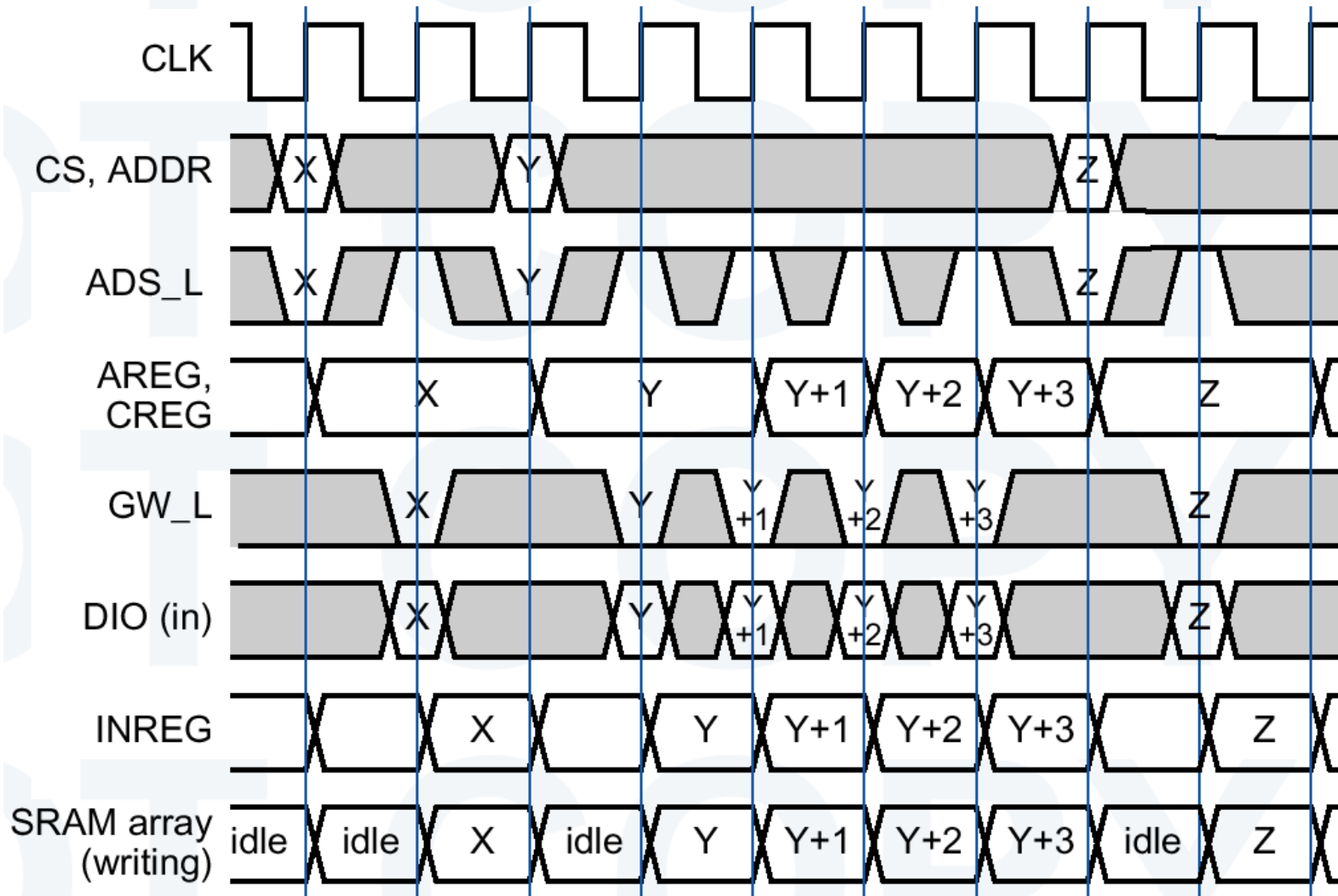

# Read SSRAM - Pipelined

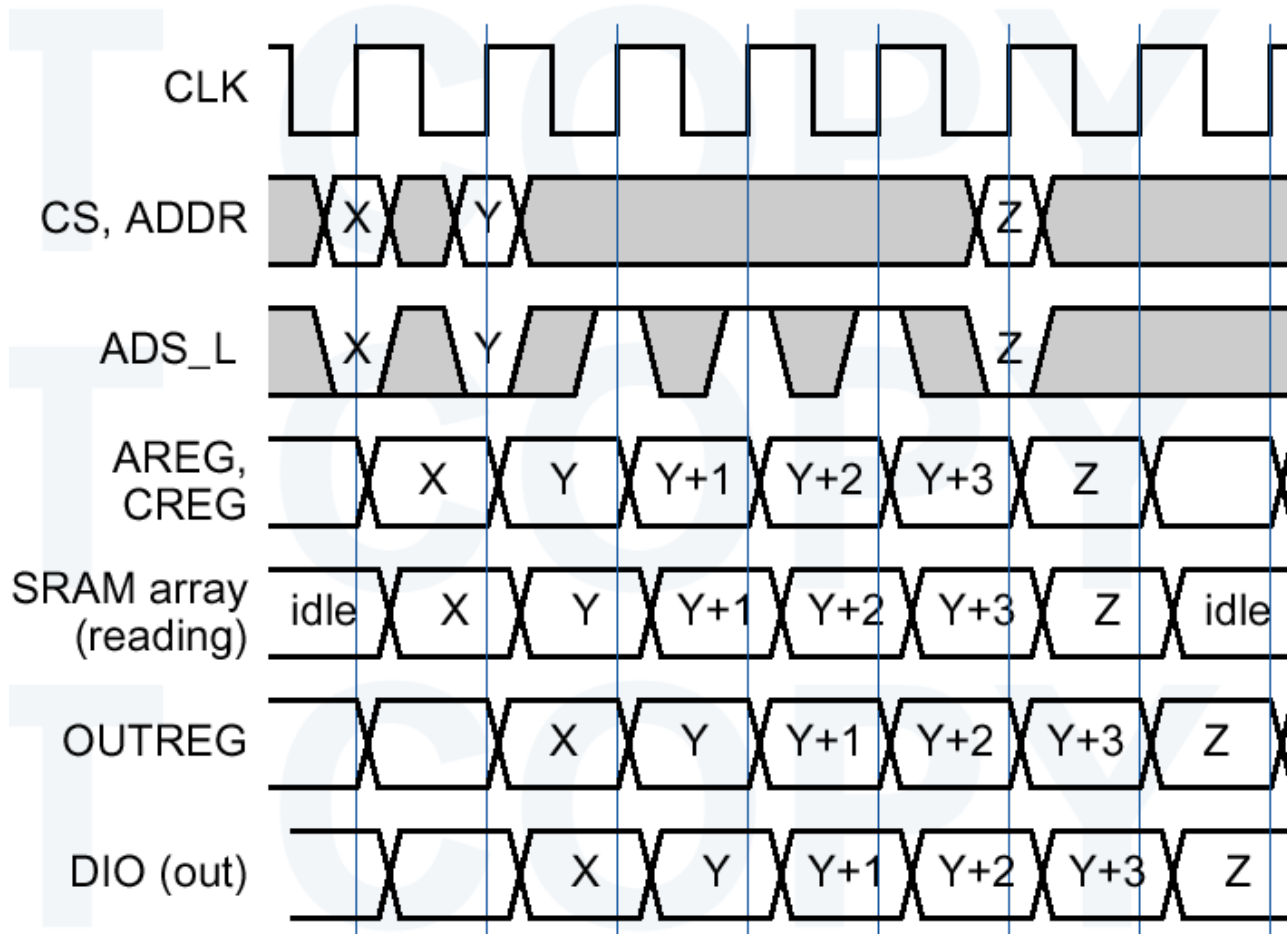

# SSRAM - Pipelined Output

- OUREG is placed between array and device outputs
  - Disadvantage: Output data is delayed by one clock
  - Advantage: Data is available for one clock period
- No change in write cycles
- Provides better setup time for device performing reads


# SSRAM -ZBT

- Late write SSRAMs suffer from one clock delay when a read follows a write or vice-versa
  - Internal SRAM array remains idle
- Turn around penalty is avoided in Zero Bus Turnaround (ZBT) SSRAMs
- The type of operation is selected by R/W\ that is sampled at the same edge of the address
- DIO bus is used for both operations
  - OE avoids bus conflicts between successive cycles




# Comparison of read to write transition

## Standard SyncBurst SRAM

 


## ZBT SRAM

 

- (1) The shaded sections represent no-operation cycles.

# SSRAM - ZBT

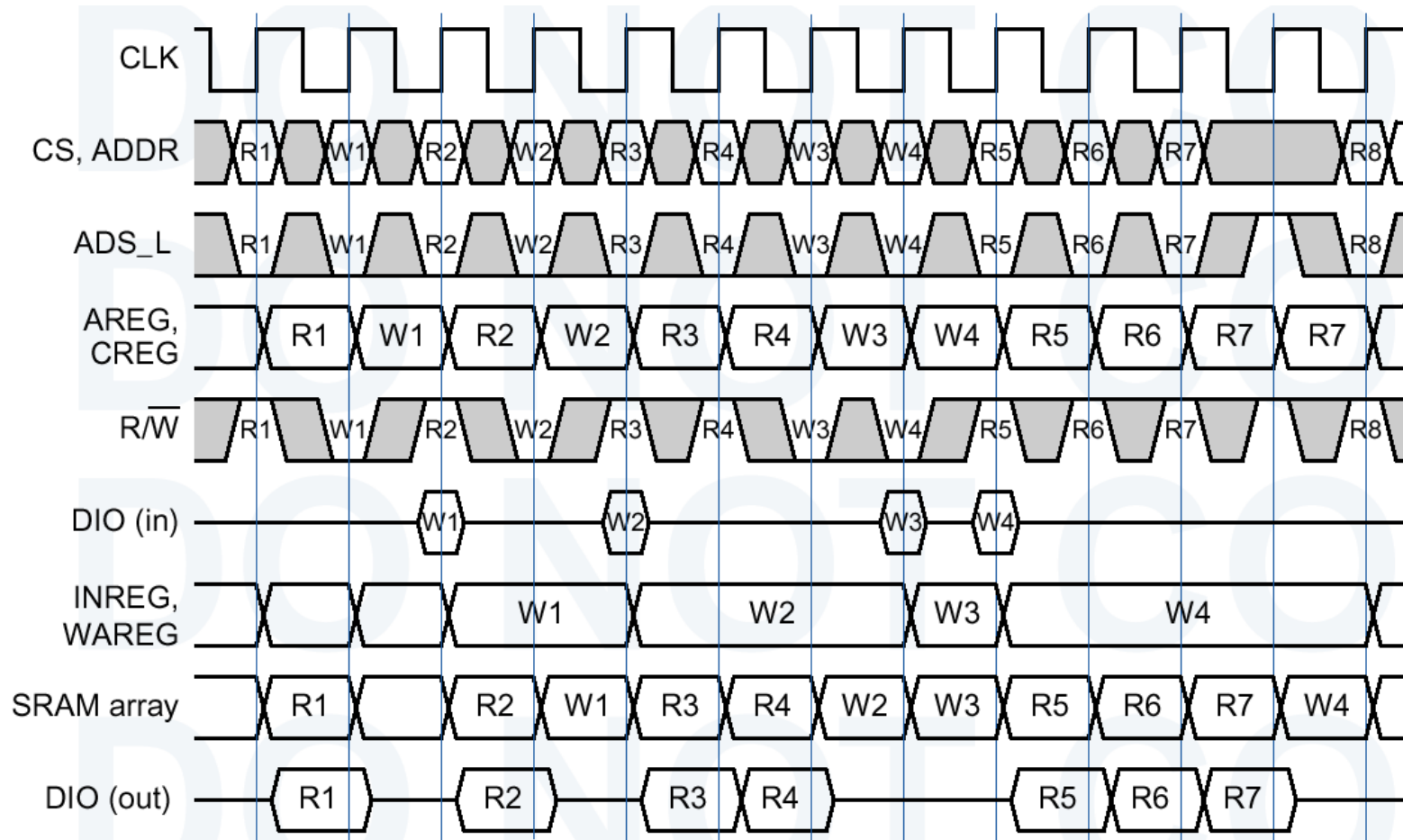

# ZBT SSRAMs


- If a write is followed by read, resource conflict for the array occurs.
  - So write operation is delayed till next available cycle
  - Opportunity occurs during a write or no operation
- While write is pending, address and data needs to be stored in another set of registers
- A write operation may be delayed indefinitely, if a series of reads follows.
  - Care should be taken if one of the reads has same address as a pending write

# QDR SSRAM


- Capable of transferring up to 4 words of data per clock
  - Both – rising and falling edges of clock
  - two clocks, one for read data and one for write data
  - separate read and write data buses
- Designed for high-speed communications and networking applications
  - Data throughput is more important than cost, power efficiency or density
  - Useful where reads and writes are interleaved
 
# DRAM (Dynamic RAMs)

- SRAMs typically use six transistors per bit of storage.
- DRAMs use only one transistor per bit:
- 1/0 is capacitor charged/discharged



# DRAM read operations

 


- Precharge bit line to  $V_{DD}/2$ .
- Take the word line HIGH.
- Detect whether current flows into or out of the cell.
- Note: cell contents are destroyed by the read!
- Must write the bit value back after reading.

# DRAM Internal Structure - Read


1. Bit Line precharged to half-high voltage

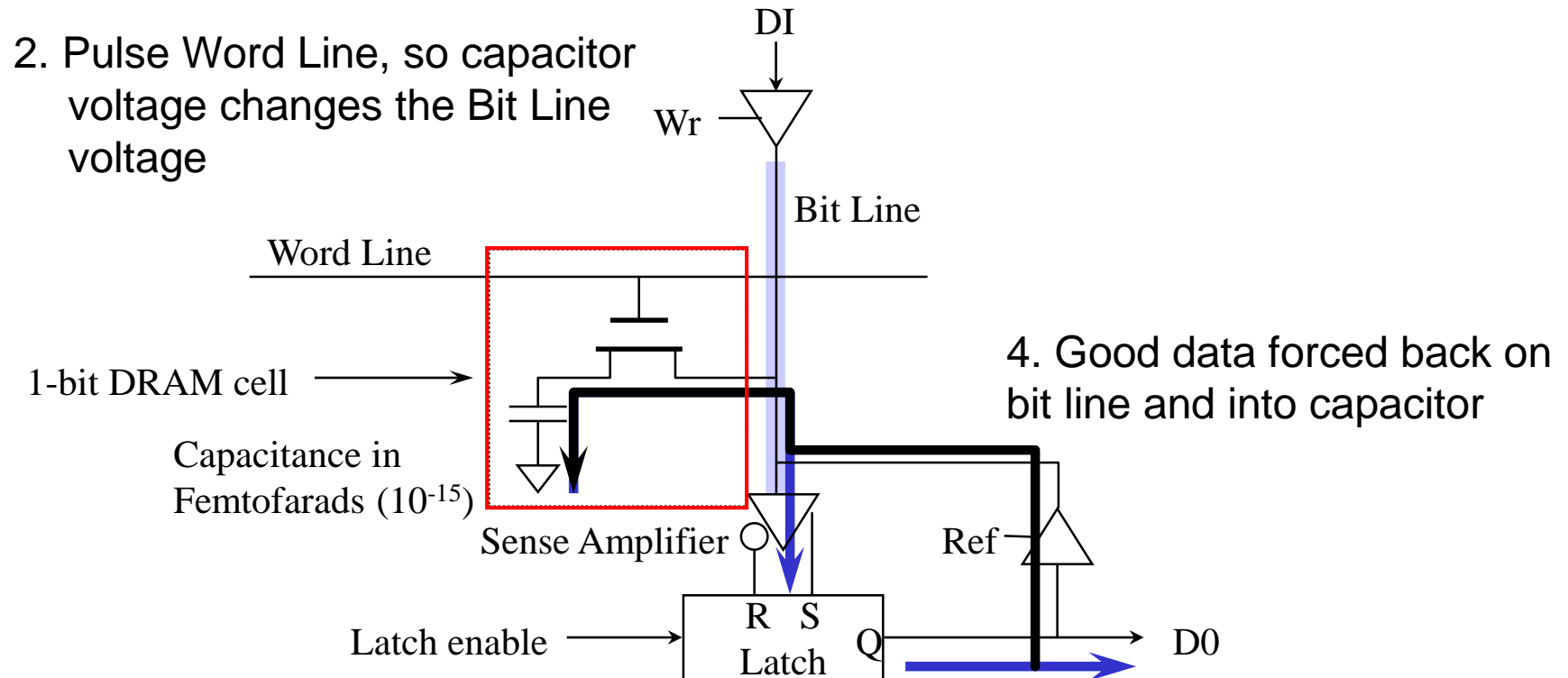2. Pulse Word Line, so capacitor voltage changes the Bit Line voltage



3. Sense Amplifier detects voltage change and latches

# DRAM write operations

 


- Take the word line HIGH.
- Set the bit line LOW or HIGH to store 0 or 1.
- Take the word line LOW.
- Note: The stored charge for a 1 will eventually leak off.



# DRAM Internal Structure - Write

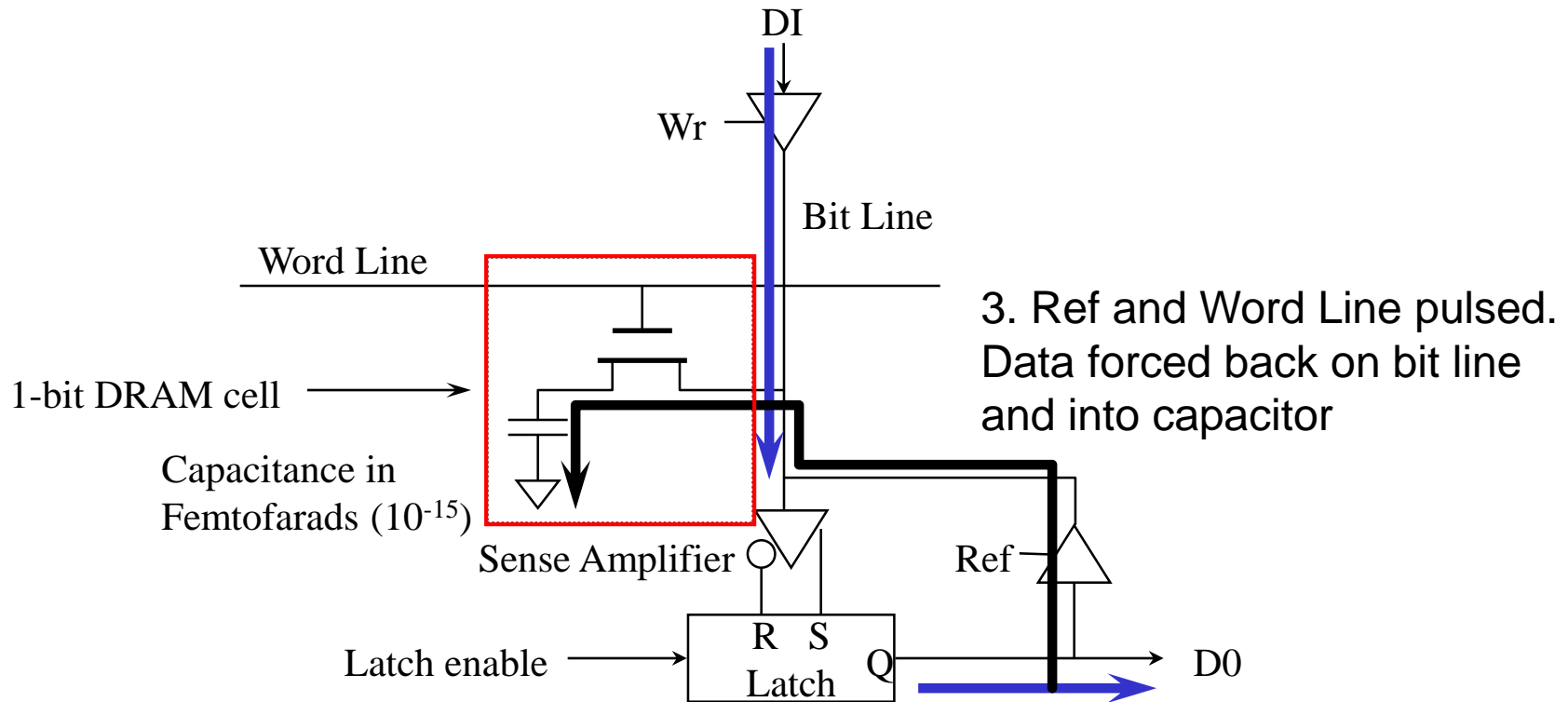
1. Drive Data onto Bit Line (enable  $W_r$ )



2. Sense Amplifier detects Bit Line and latches new data
 
# Cell Voltage Discharge and Refresh

- Capacitor stores a charge for several milliseconds. Why so short?
- So we must re-write or refresh every cell voltage within 4 ms (typically)




# Refresh Cycles overheads


- Each refresh cycle takes time away from useful read/write cycles
- Any useful time left for reading or writing data?
  - Refresh entire row in 1 cycle
  - Typically 256 rows in a DRAM refreshed sequentially
  - Assume 1 refresh cycle takes  $\approx 100$  ns
  - What percentage of time is available for read/write cycles?
    - $4\text{ms}/256 \gg 16$  us per row refresh
    - $0.1/16 < 1$  % of time used for refresh cycles
    - so  $\gg 99$  % of time remains for read/write cycle
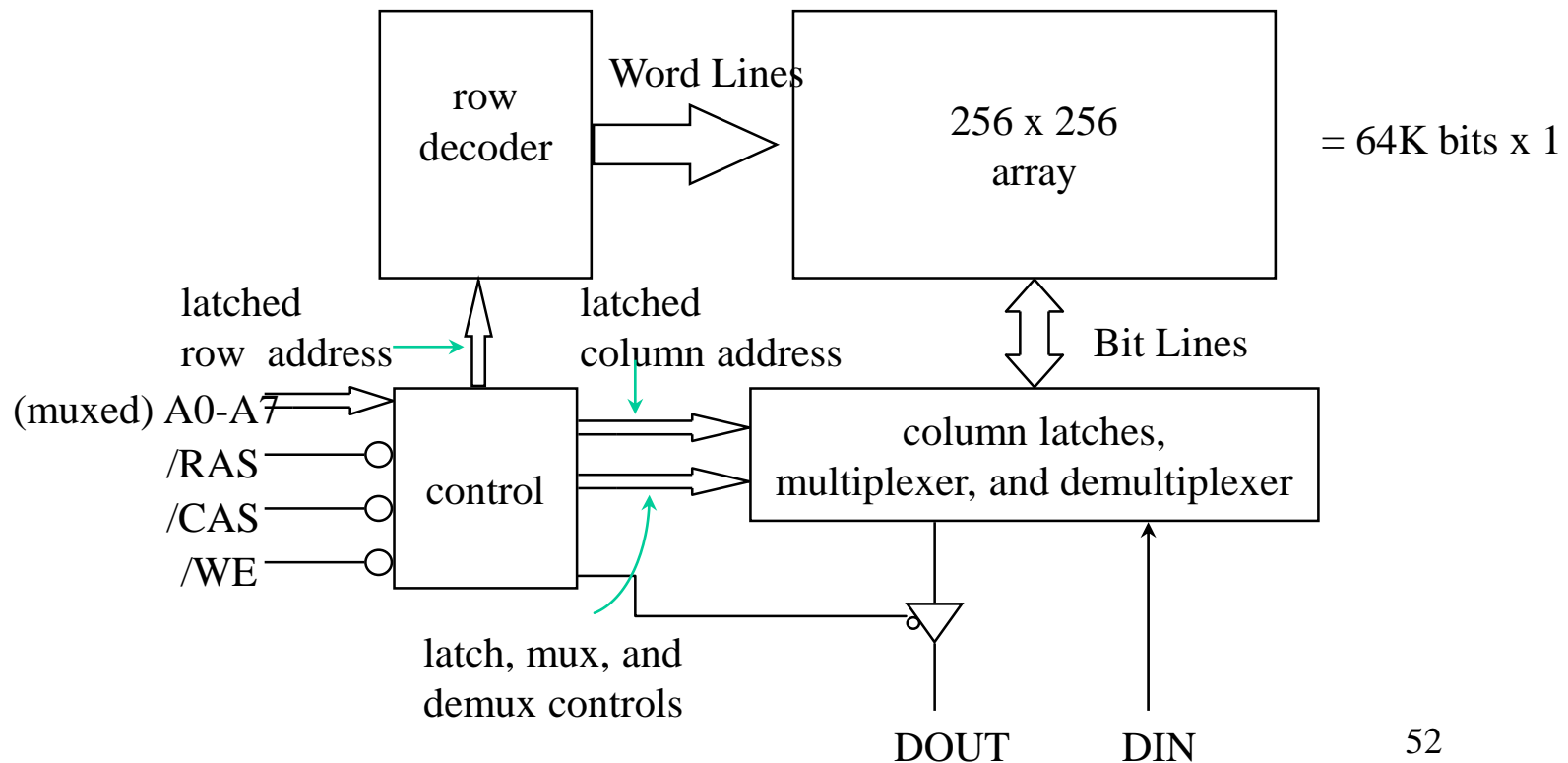
# Structure of 64K x 1 DRAM


- 16 bit Address multiplexed into two 8-bit load operations
- 8 bit Row Address latched during /RAS pulse
- 8 bit Column Address latched during /CAS pulse



# DRAM Timing: Read

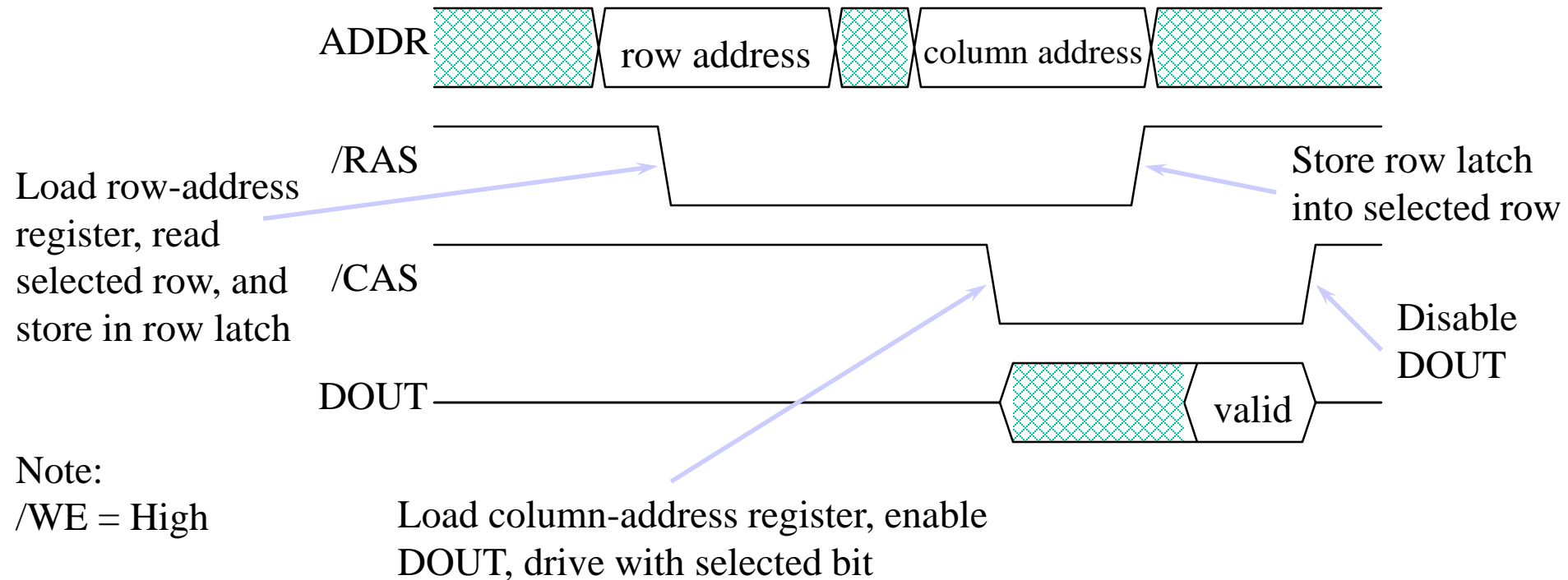

# Read Cycle DRAM-Read

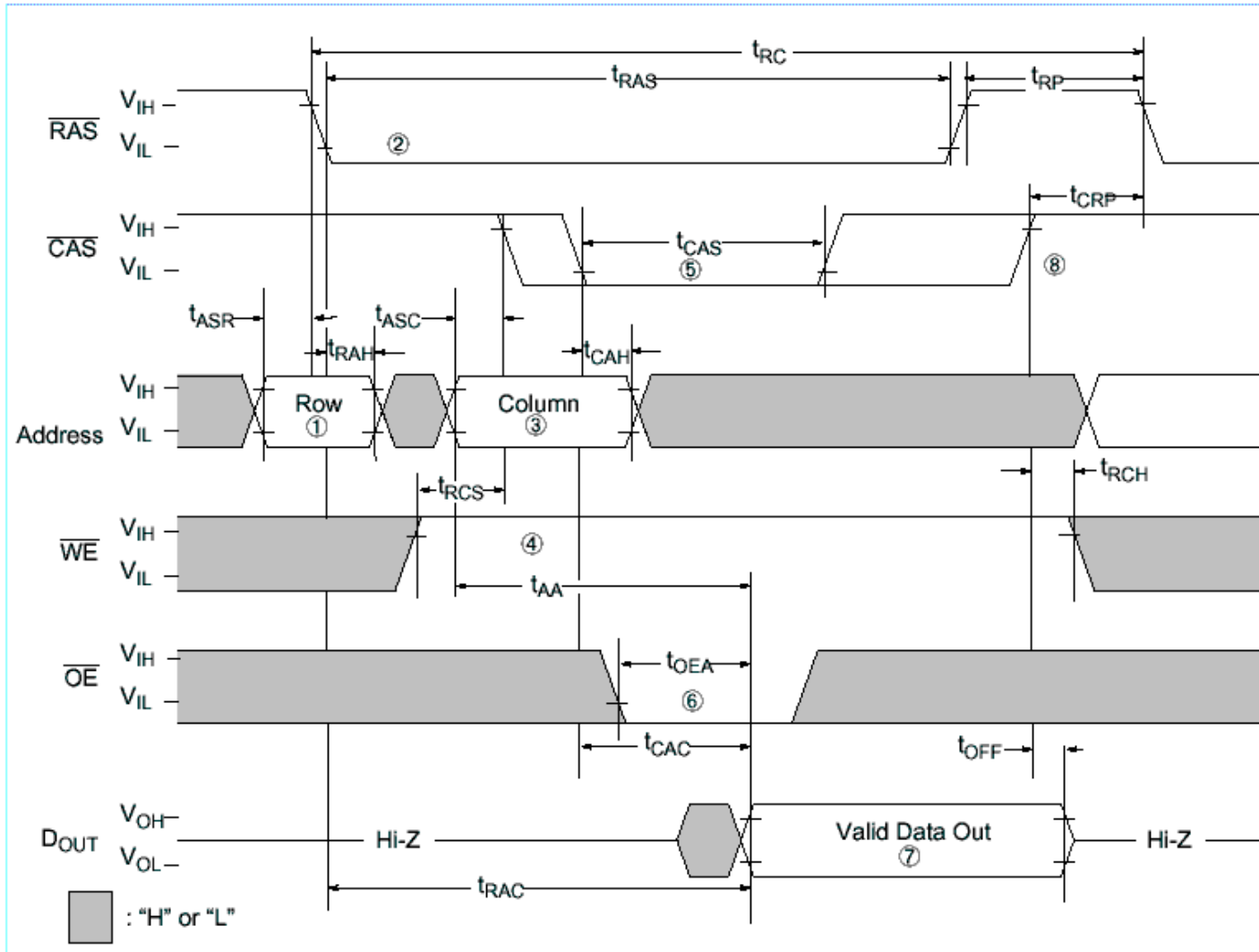

# DRAM Timing: Read Cycle


- /WE kept high
- /RAS (falling edge)
  - Latches address into Row Address Latch
  - All bit lines precharged to intermediate voltage
  - 1 word line activated from Row Address
  - Bit Line voltage slightly changed +/- by capacitor charge
  - Sense amplifiers store data in Row Data Latch when enabled
- /CAS (falling edge)
  - Latches column address into Column Address Latch
  - Selects 1 bit of Row Data Latch with a MUX to drive DOUT
  - Enable DOUT tri-state buffer to output data (like OE in SRAM)

# DRAM Timing: Read Cycle

- /RAS (rising edge)
  - Row Data Latch driven back onto bit lines when **ref** signal active
  - Selected row of cells re-written High or Low
  - Word Line de-activated
- /CAS (rising edge)
  - Disable DOUT tri-state buffer



# DRAM Timing: Write

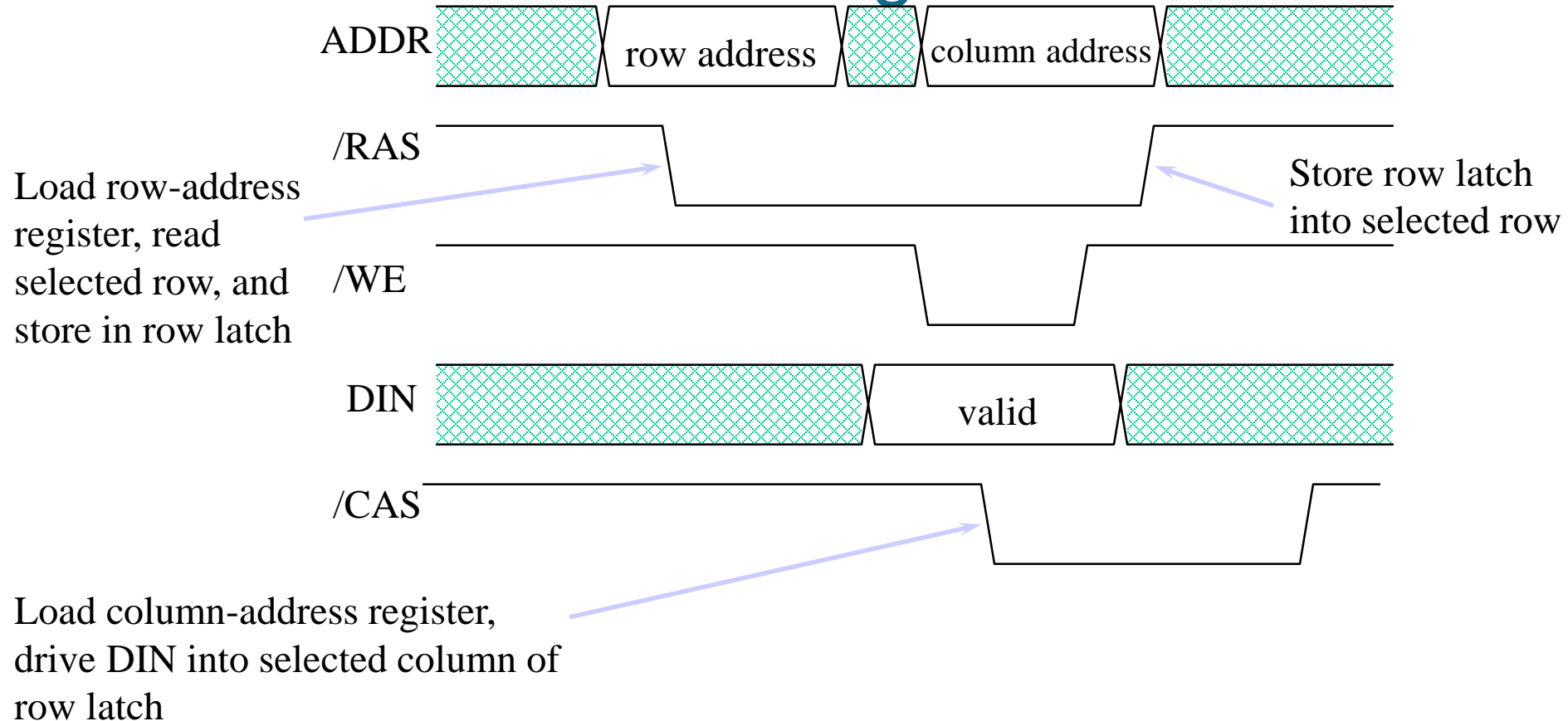

Note: DOUT = Hi-Z


# DRAM Timing: Write Cycle

- /RAS (falling edge)
  - Latches address into Row Address Latch
  - All bit lines precharged to intermediate voltage
  - 1 word line activated from Row Address
  - Bit Line voltage slightly changed +/- by capacitor charge
  - Sense amplifiers store data in Row Data Latch when enabled
- /CAS (falling edge) with /WE true
  - Latches column address into Column Address Latch
  - Drives DIN onto the selected Bit Line and into one Row Data Latch

# DRAM Timing: Write Cycle

- /RAS (rising edge)
  - Row Data Latch driven back onto bit lines when **ref** signal active
  - Selected row of cells re-written High or Low, with one new bit
  - Word Line de-activated
- /CAS (rising edge)
  - End of write cycle

# DRAM Timing: RAS-only Refresh

 

Load row-address register,  
read selected row, and store  
into row latch

Restore row latch  
back into selected  
row of cells


(Note: /CAS = /WE = High)

# DRAM: RAS-only Refresh Cycle

- /CAS, /WE kept high throughout cycle
- /RAS (falling edge)
  - Latches address into Row Address Latch
  - All bit lines precharged to intermediate voltage
  - 1 word line activated from Row Address
  - Bit Line voltage slightly changed +/- by capacitor charge
  - Sense amplifiers store data in Row Data Latch when enabled
- /RAS (rising edge)
  - Row Data Latch driven back onto bit lines when **ref** signal active
  - Selected row of cells re-written High or Low
  - Word Line de-activated

 
# Other Types of DRAM Cycles (1)

- CAS-before-RAS Refresh
  - Internal Row-Addr counter used and incremented
  - Eliminates external addr counter and part of Addr mux




- Read-Modify-Write
 

 Normal Read ending with WE pulse to write new data in same location - Faster


 
## Other Types of DRAM Cycles (2)


- Page Mode Read
  - Allows entire DRAM row to be output **FAST**
  - 1 RAS pulse
  - 1 CAS pulse per output bit



- Page Mode Write
  - Allows multiple bits per DRAM row written **FAST**
  - 1 CAS pulse per input bit (with /WE true)
 
# Other Types of DRAM Cycles (3)

- Static-Column-Mode Read
  - 1 long RAS pulse, 1 long CAS pulse
  - Multiple column addresses (not latched) supplied for multiple output bits





# DRAM Types

DRAM – Dynamic Random Access Memory

Normally Asynchronous

EDORAM – Extended Data Output RAM

Outputs are registered

FPMDRAM – Full Page Access DRAM

Give row only once go on changing column

SDRAM – Synchronous DRAM

DRAM based on Clock


ESDRAM – Enhanced Synchronous DRAM

Small SRAM on same chip

RDRAM – Rambus® DRAM

Protocol based proprietary
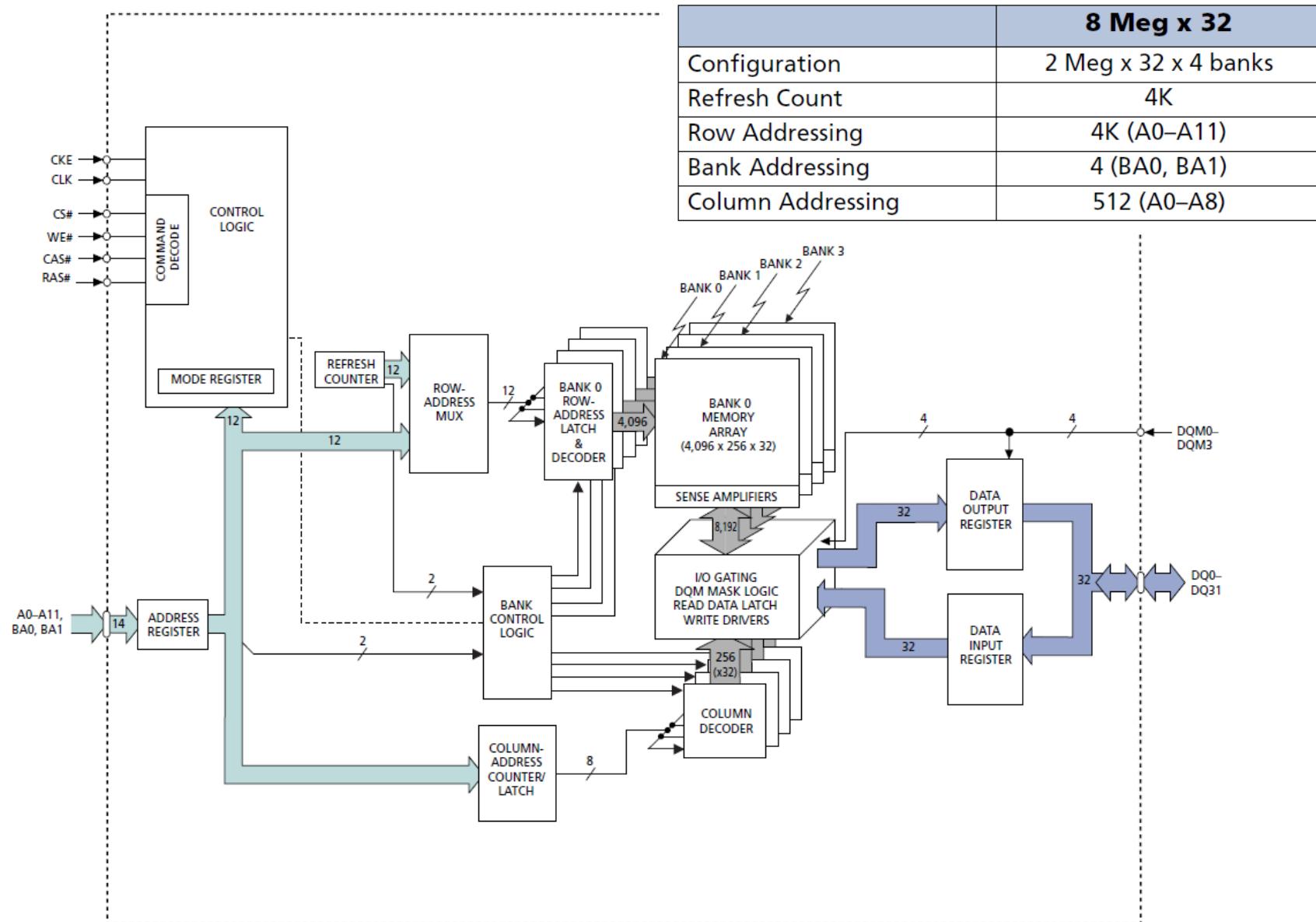
# Functional Block Diagram – 8 Meg x 32 SDRAM



# SDRAM

- All signals are latched on positive edge of clock
- Internally, divided into multiple banks
- Read and write access are burst oriented
- Access begins with registration of ACTIVE command
  - Followed by a READ or WRITE command
- The address bits registered coincident with the ACTIVE command are used to select the bank and row to be accessed
- The address bits registered coincident with the READ or WRITE command are used to select the starting column location for the burst access

# SDRAM

- Provision for programmable READ or WRITE burst lengths of 1, 2, 4, or 8 locations, or the full page, with a burst terminate option.
- Precharging one bank while accessing one of the other banks will hide the precharge cycles and provide seamless, highspeed, random-access operation.
- Prior to normal operation, the SDRAM must be initialized.

# SDRAM Commands

NAME (FUNCTION)	CS#	RAS#	CAS#	WE#	DQM	ADDR	DQS
COMMAND INHIBIT (NOP)	H	X	X	X	X	X	X
NO OPERATION (NOP)	L	H	H	H	X	X	X
ACTIVE (Select bank and activate row)	L	L	H	H	X	Bank/Row	X
READ (Select bank and column, and start READ burst)	L	H	L	H	L/H <sup>8</sup>	Bank/Col	X
WRITE (Select bank and column, and start WRITE burst)	L	H	L	L	L/H <sup>8</sup>	Bank/Col	Valid
BURST TERMINATE	L	H	H	L	X	X	Active
PRECHARGE (Deactivate row in bank or banks)	L	L	H	L	X	Code	X
AUTO REFRESH or SELF REFRESH (Enter self refresh mode)	L	L	L	H	X	X	X
LOAD MODE REGISTER	L	L	L	L	X	Op-Code	X
Write Enable/Output Enable	–	–	–	–	L	–	Active
Write Inhibit/Output High-Z	–	–	–	–	H	–	High-Z

# DDR SDRAM

- Double Data Rate SDRAM is advantageous for systems that require higher bandwidth than can be obtained using SDRAM.
- Enhancements to the SDRAM core
  - Prefetching
  - double transition clocking
  - strobe-based data bus,
  - SSTL\_2 low voltage signaling.
- At 400 MHz, DDR increases memory bandwidth to 3.2 GB/s, which is 400 percent more than original SDRAM.

# Pre-fetching

- In SDRAM, one bit per clock cycle is transferred from the memory cell array to the input/output (I/O) buffer or data queue (DQ).
- The I/O buffer releases one bit to the bus per pin and clock cycle
- Pre-fetching transfers two bits from the memory cell array to the I/O buffer in two separate pipelines.
- Then the I/O buffer releases the bits in the order of the queue on the same output line.
- This is known as a  $2n$ -prefetch architecture because the two data bits are fetched from the memory cell array before they are released to the bus in a time multiplexed manner.

# Double transition clocking

- Standard DRAM transfers one data bit to the bus on the rising edge of the bus clock signal,
- DDR SDRAM uses both the rising and falling edges of the clock to trigger the data transfer to the bus
- This, double transition clocking, delivers twice the bandwidth of SDRAM without increasing the clock frequency.



## SSTL\_2 & Strobe-based data bus

- Instead of using a 3.3-V operating voltage, DDR SDRAM uses a 2.5-V signaling specification known as Stub Series-Terminated Logic<sub>2</sub>
- This low-voltage signaling results in lower power consumption and improved heat dissipation.
- SSTL<sub>2</sub> signaling allows DDR SDRAM to run at faster speeds than traditional SDRAM.
- DDR SDRAM uses a delay-locked loop (one for every 16 outputs) to provide a data strobe signal as data becomes valid on the SDRAM pins.
- The memory controller uses the data strobe signal to locate data more accurately and resynchronize incoming data from different DIMMs.

# Summary of DDR SDRAM

Type	Component naming convention	Module naming convention	Bus speed	Peak bandwidth
DDR	DDR200	PC1600	100 MHz	1.6 GB/s
	DDR266	PC2100	133 MHz	2.1 GB/s
	DDR333	PC2700	166 MHz	2.7 GB/s
	DDR400	PC3200	200 MHz	3.2 GB/s
DDR-2	DDR2-400	PC2-3200R	200 MHz	3.2 GB/s
	DDR2-533	PC2-4300	266 MHz	4.3 GB/s
	DDR2-667	PC2-5300	333 MHz	5.3 GB/s
	DDR2-800	PC2- 6400	400 MHz	6.4 GB/s

# SDR and DDR

- Single Data Rate SDRAM can accept one command and transfer one word of data per clock cycle.
  - 168-pin DIMMs read or write 64 (non-ECC) or 72 (ECC) bits at a time.
- DDR SDRAM uses the same commands, accepted once per cycle, but reads or writes two words of data per clock cycle.
- The supply voltage is reduced from 3.3 to 2.5 V.
- It doubles the minimum read or write unit; every access refers to at least two consecutive words.
- Typical DDR SDRAM clock speeds are 133, 166 and 200 MHz generally described as DDR-266, DDR-333 and DDR-400
  - Corresponding 184-pin DIMMS are known as PC2100, PC2700 and PC3200.

# DDR2 and DDR3

- DDR2 doubles the minimum read or write unit again, to 4 consecutive words.
- The bus speed of the SDRAM is doubled without increasing the speed of internal RAM operations
  - internal operations are performed in units 4 times as wide as SDRAM.
- Typical DDR2 SDRAM clock speeds are 200, 266, 333 or 400 MHz generally described as DDR2-400, DDR2-533, DDR2-667 and DDR2-800
  - Corresponding 240-pin DIMMS are known as PC2-3200 through PC2-6400
- DDR3 continues the trend, doubling the minimum read or write unit to 8 consecutive words. This allows another doubling of bandwidth and external bus speed without having to change the speed of internal operations.

# Cache

# Memory Requirements

- Programmers want unlimited amount of fast memory
- Hardware aids programmer by creating an illusion of unlimited fast memory
- Realities
  - Fast memory is costly
  - Programs tend to follow principle of locality
    - Temporal: same location is repeatedly accessed
    - Spatial: Close by locations are accessed soon

# Processor and memory speeds

- When microprocessors were introduced, standard memory parts were faster than contemporary microprocessors
- Over a period
  - Microprocessors have become faster
  - Memories have become little faster but mostly have higher capacity
- The memories are not able to keep up with the speed achieved by microprocessors

# How to bridge the gap

- Interleaving the memory
  - High bit interleaving (mainly used to increase memory size)
  - Low bit interleaving (used to overlap memory delays and speedup the operations)
- Wider memory paths
- Cache memory system




# Memory Hierarchy

- Takes advantage of principle of locality
- Memory subsystem consists of multiple levels with different speeds and sizes.
- Small fast memory is put close to processor and slower away
- The goal
  - Provide maximum memory which is cheapest
  - Provide access at the speed offered by the fastest
- Data is copied only between two adjacent levels
- If data is found in level closest to CPU, it's a hit
- Hit rate is a measure of the performance

# Speed of Memory

- Registers
  - 10s in number ; 1 - 5 ns access time
- Fast SRAMs
  - 1k - 10k ; 10-20ns
- SRAMs
  - 10k to few MB ; 20-40ns
- Main memory
  - 100MB to 1GB; 50-100 of ns
- Magnetic storage
  - 10G to 500G; 10 msecs


# Memory Hierarchy

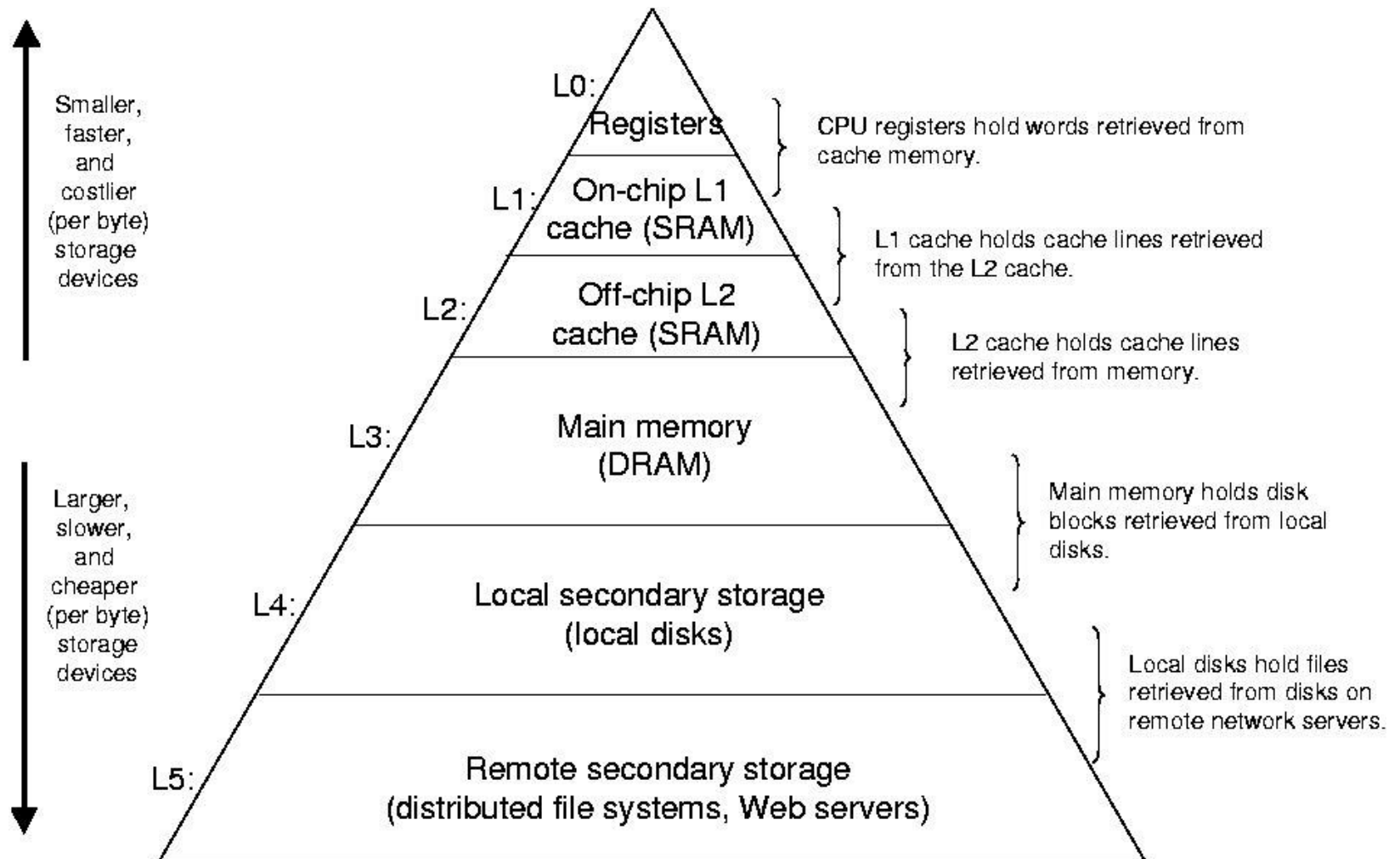

# Cache

Cache: as safe place for hiding or storing things

-Webster's New world dictionary

 


- Cache contains a copy of portions of main memory
- When CPU attempts to read a word, cache is checked first. If found, it is presented, else a line of words is brought from main memory to the cache

# Basic Architecture of Cache

- A cache consists of 3 main parts
  - Directory store
    - The cache must know where the information in cache originated from
    - Each directory entry is called as cache-tag
  - Data section
    - Holds the data copied from main memory
  - Status information
    - Valid bit indicates live data
    - Dirty bit indicates non-coherency


# Inside a Cache

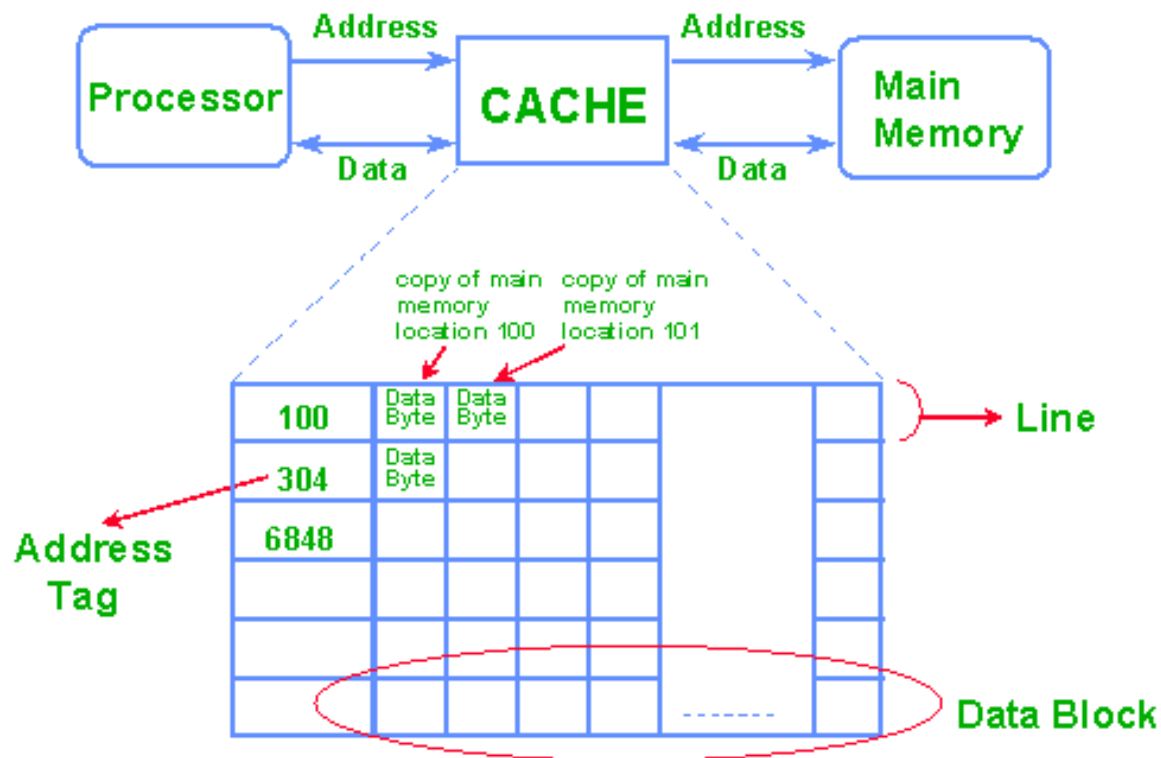

# Cache Controller

- It's the hardware that copies code or data from main memory to cache memory automatically.
- The operation is transparent to CPU and the software
- It intercepts reads and writes before passing them on to the memory controller.
- The relationship between main memory and cache is called as mapping

# Cache Read Algorithm

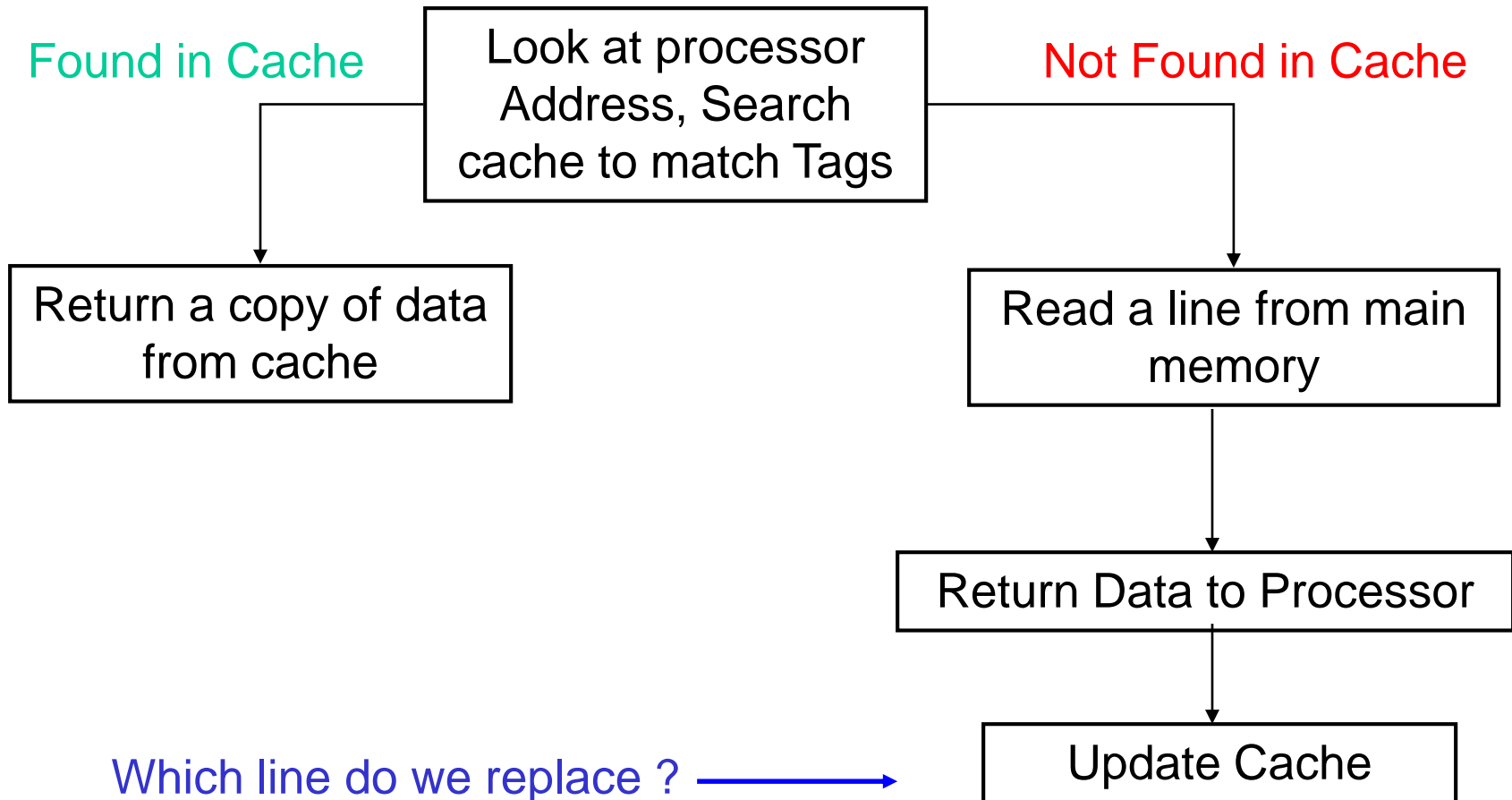




# Cache Mapping

- Mapping between main memory locations and cache
  - Direct mapped
  - N-way set-associative ( $n=2,4$ )
  - Fully set-associative


# Direct mapped

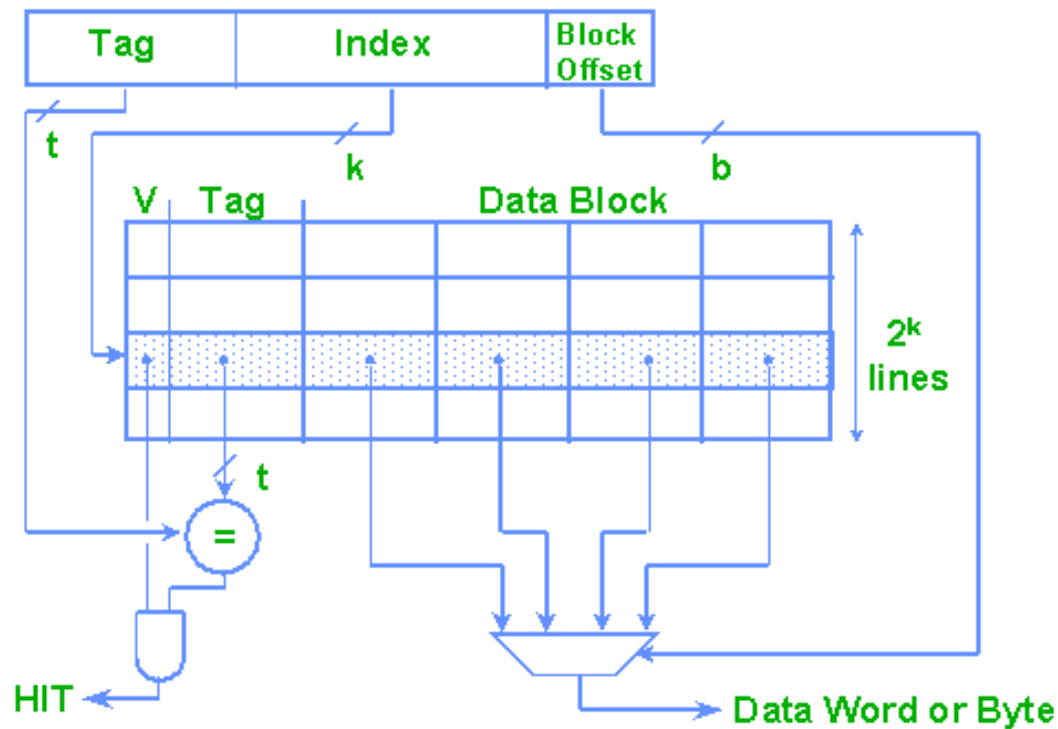

# Direct Mapped Cache

- Address is broken into 3 parts
  - Bottom ‘b’ bits correspond to offset with the line
  - Next ‘k’ bits access an entry into the cache
  - Top ‘t’ bits act as a tag
- Replacement policy is simple to implement
  - Each memory location has only destination in cache
- Disadvantage is – if two memory lines are used alternatively, which map onto the same cache line, the hit ratio will sharply drop


# 2-way Set Associative Cache

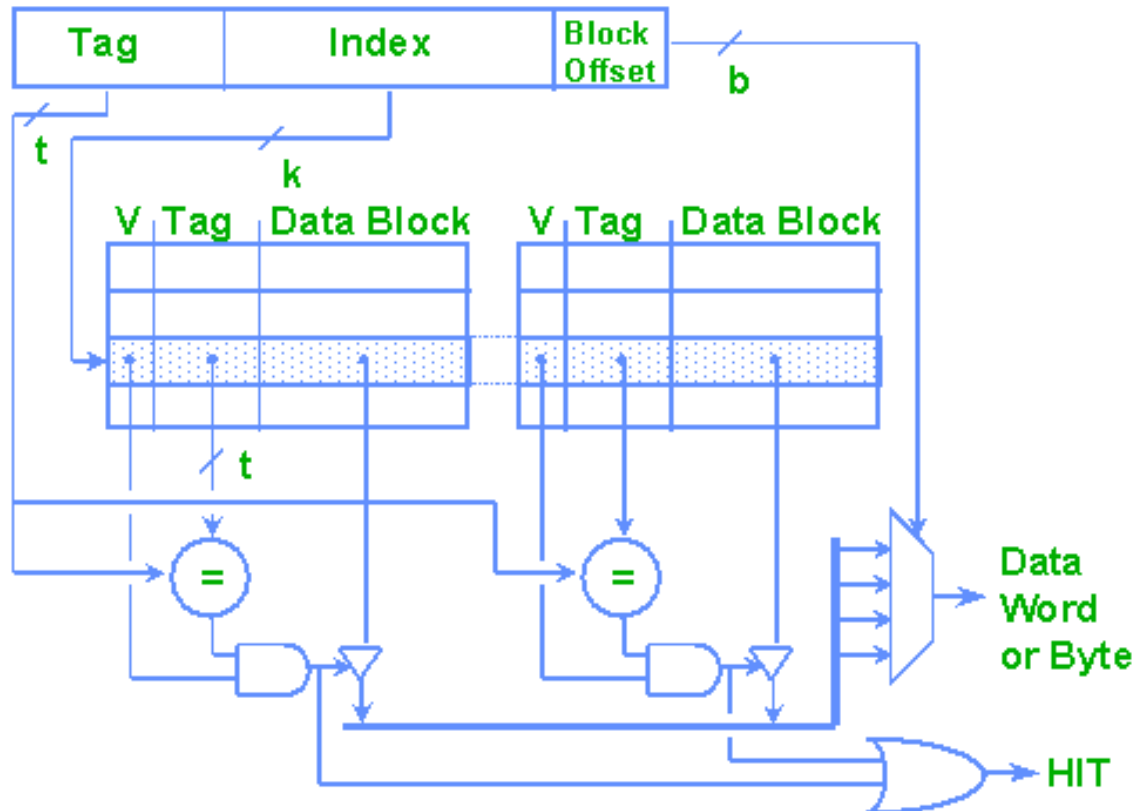

## 2-way Set Associative Cache

- Improved direct mapped cache
- Each memory line has two destinations in cache
- Extra logic is required for comparing tags
- Replacement policy needs consideration


# Fully Associative Cache

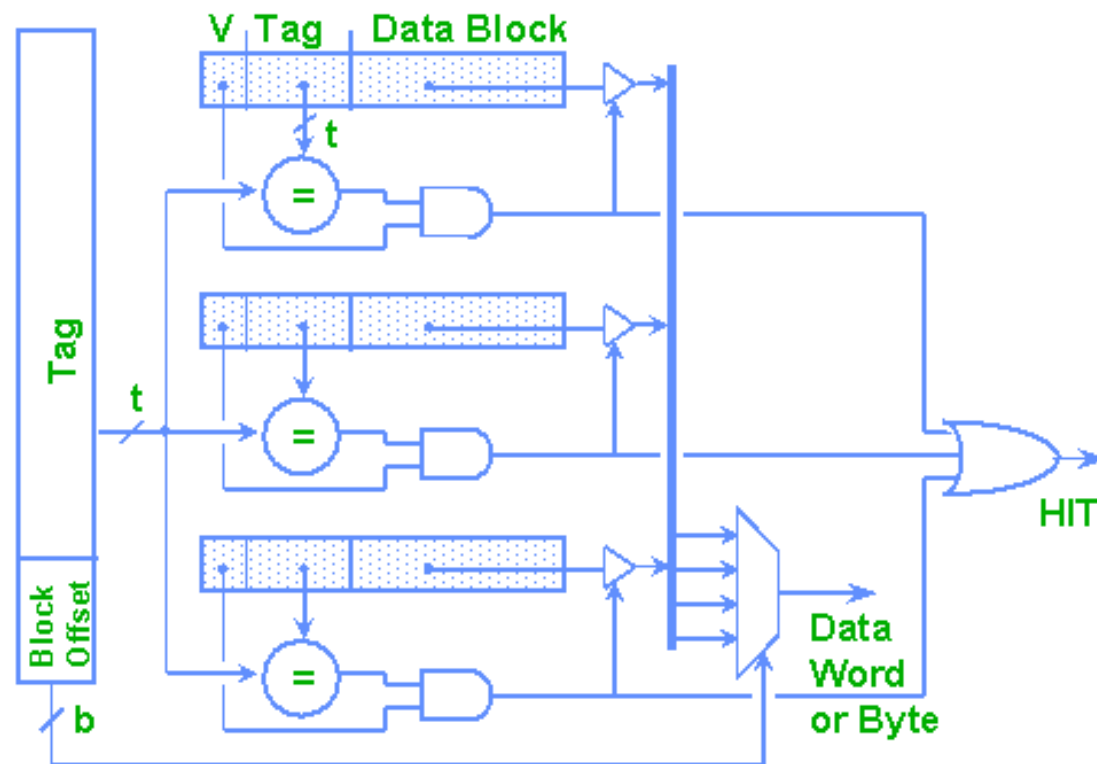

# Fully Associative Cache

- This scheme represents other extreme
  - Any line can be placed in any location in cache
- Gives highest hit ratio
- Search is slowest
- Content addressable Memories (CAM) are used for storing Tags

# Valid bits

 

- Valid bit must be **1** for cache line to **HIT**.
- At power-up or reset, we set all valid bits to **0**.
- Set valid bit to **1** when cache line is first replaced.
- Flush cache by setting all valid bits to **0**, under external program control.



# Cache Efficiency

- Two terms are use to characterise cache efficiency of a program
  - Cache hit rate
  - Cache miss rate

$$\text{Hit rate} = \frac{\text{cache hits}}{\text{memory requests}} \times 100$$

- Rates can measure read, writes or both
- Other performance measurement terms are hit time and miss penalty

# Cache Policy

- Three policies determine cache operation
  - Write policy
    - Determines where data is stored during processor write operation
  - Replacement policy
    - Determines the line that will be used for next line fill during a cache miss
  - Allocation policy
    - Determines when the cache controller allocates a line


# Cache Coherency Problem

- It arises when the data in the cache is different as compared to the data in the main memory. Stale data.
- This problem is of concern only when there is more than one entity using the memory. e.g. multiprocessor systems, systems with DMA agents.
- To avoid the problem write-through policy is used.
- The cache controller snoops the memory bus for memory operations and updates the cache whenever required. This is called as snooping.

# Write Policy

- Two alternatives when processor issues a write
  - Update both cache and main memory: **write-through**
  - Update only the cache: **write-back**
- Write-through
  - Both memories remain coherent all the time
  - Writes are slower
- Write-back
  - Valid cache lines and memory may not be coherent
  - Dirty bits are used to indicate non-coherency
  - Dirty cache line are updated before eviction

# Dirty bits for write-back caches

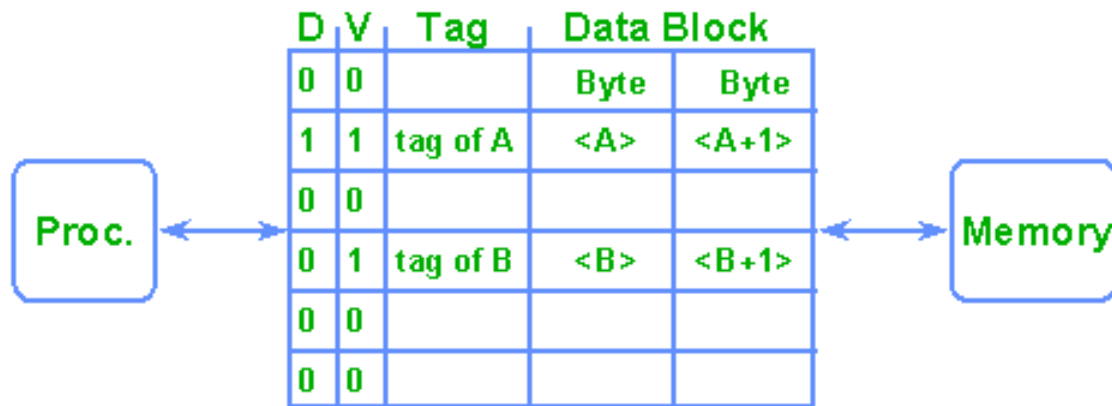

When the line corresponding to **A** is replaced, its data block has to be written to main memory since its dirty bit is set.

# Replacement Policy

- After a read miss, which cache line should be replaced with the data line read from main memory
  - Direct mapped cache: unique line
  - Associative cache
    - Least Recently Used(LRU): Replace line in set corresponding to address which has not been read or written for the longest time
    - First-in First Out(FIFO): Select line which has been in the set for the longest time
    - Random: Select line in the set randomly

# Allocation Policy

- Two strategies to allocate cache line on a cache miss
  - Read-allocate
    - Allocation is done during read from main memory
    - A write does not update cache unless a line was allocated on previous read
  - Read-write-allocate
    - Allocation is done during either a read or write
    - On write, if cache line is not valid, it does a cache fill before updating the cache.
  - Write policy determines whether main memory should be updated

# Thank You

ashishk @ cdac.in